

Chapter 27 Circuits

Objective

27-1 Pumping Charges
27-2 Work, Energy, and EMF
27-3 Calculating the Current in a Single-Loop Circuit
27-4 Potential Differences
27-5 Resistances in Series and in Parallel
27-6 Multiloop Circuits
27-7 RC Circuits

27-1 Pumping Charges Emf devices

Battery
Electric generator
Solar cell

Devices that maintain potential difference between their terminals by doing work on charge carriers.


These devices are called **emf devices**

Emf is an outdated phrase which stands for electromotive force

An emf device provides an emf \mathcal{E}


27-2 Work, Energy, and EMF

Battery

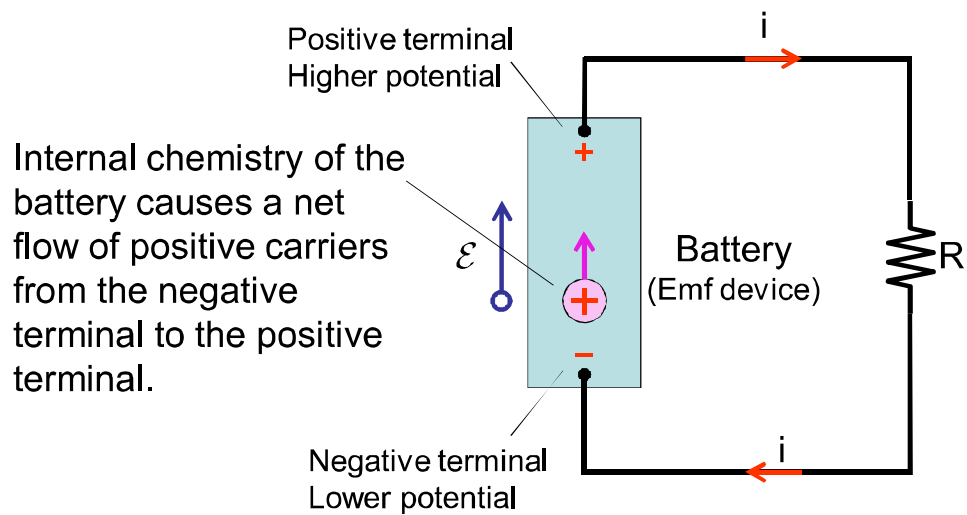


27-2 Work, Energy, and EMF

Sources of energy in emf devices

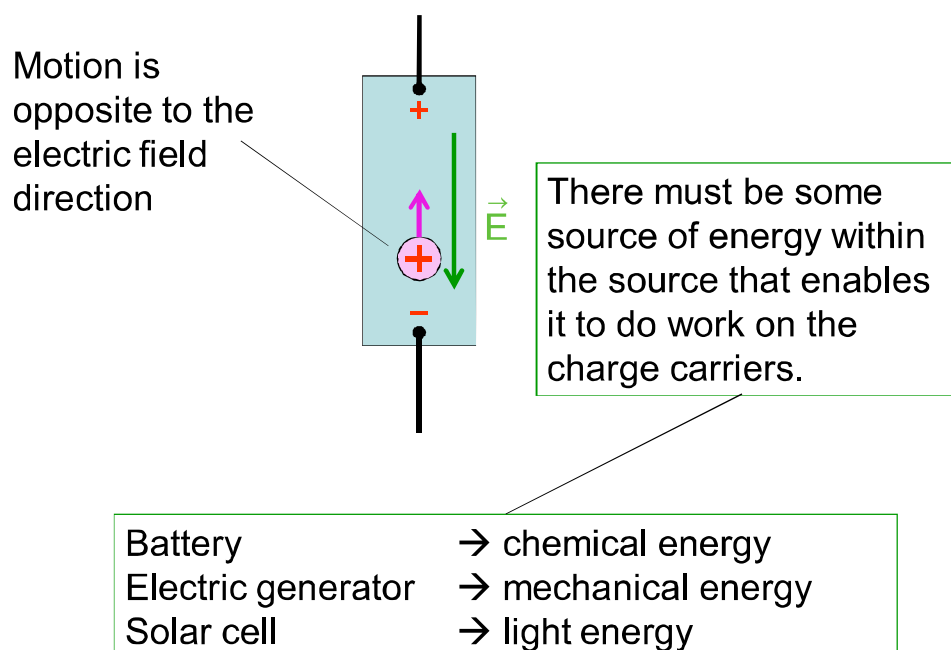

27-2 Work, Energy, and EMF

Formula - Emf

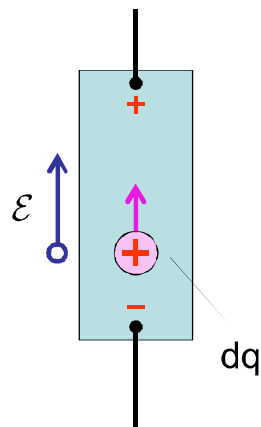

$$\mathcal{E} = \frac{dW}{dq}$$



The emf \mathcal{E} of an emf device is the work per unit charge that an emf device does in moving charge from its lower-potential terminal to its higher-potential terminal.

\mathcal{E} is measured in $\frac{\text{Joule}}{\text{Coulomb}} = \text{Volt}$

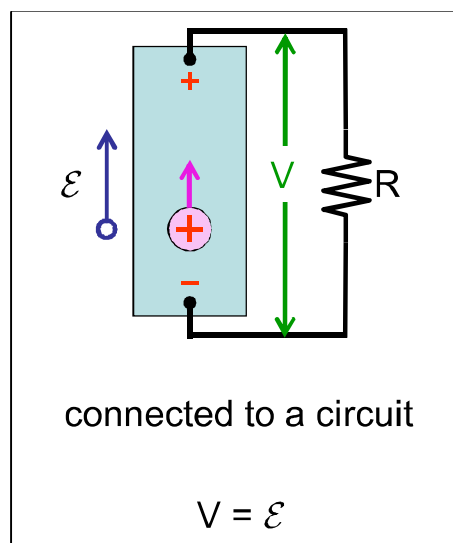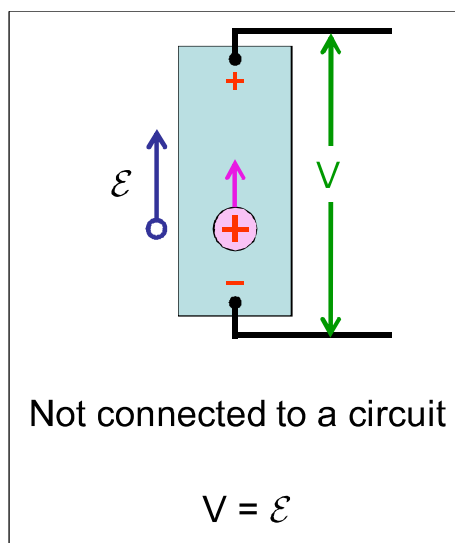27-2 Work, Energy, and EMF

Ideal emf devices

Ideal emf devices have **no** internal resistance to the movement of charge.




Potential difference between the terminals = the emf of the device.

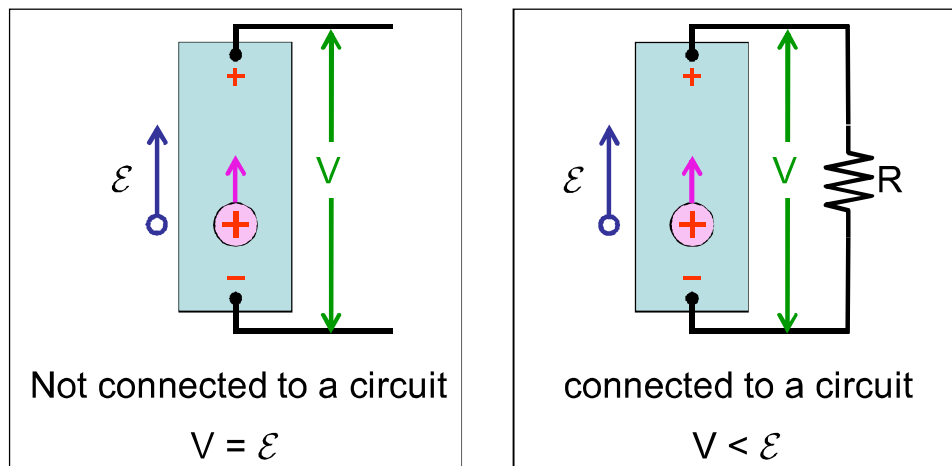27-2 Work, Energy, and EMF

Real emf devices


Real emf devices
have internal resistance to the movement of charge.



When connected to a resistor, the potential difference between the terminals $<$ the emf of the device.


27-2 Work, Energy, and EMF

Energy conversion in an electric circuit

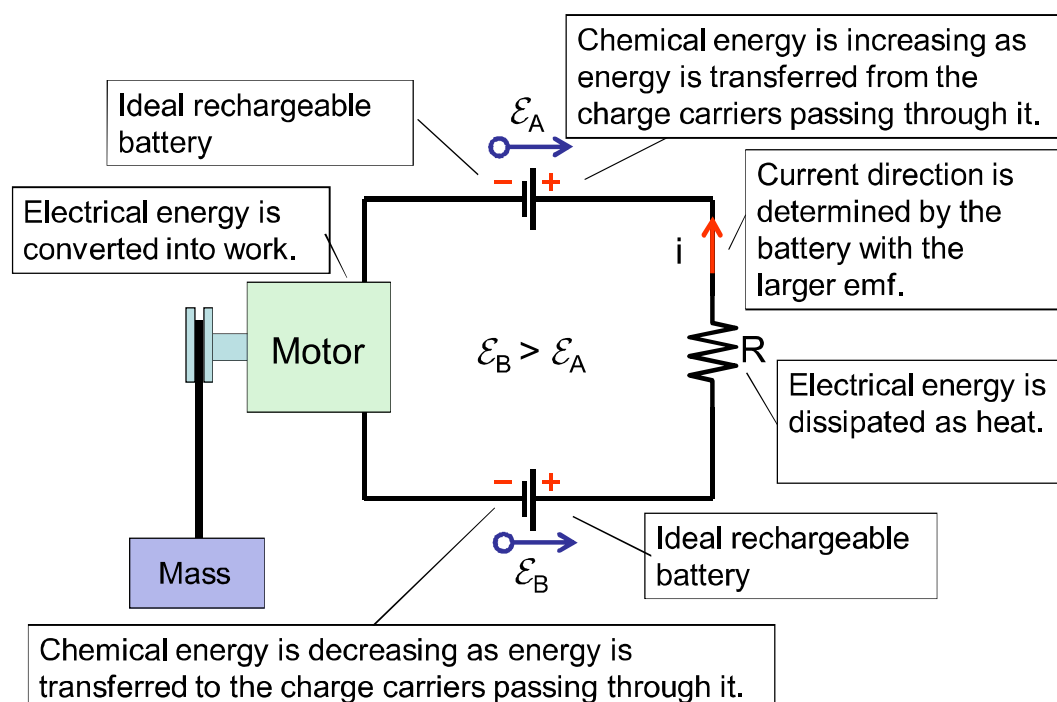

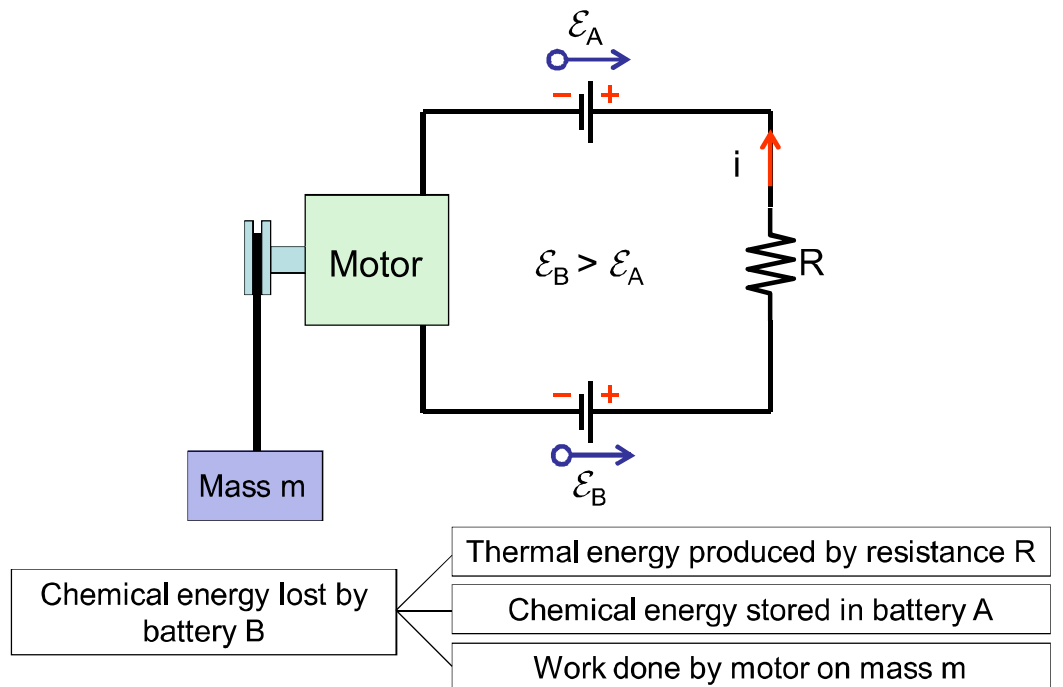27-2 Work, Energy, and EMF


Energy conservation in an electric circuit



27-3 Calculating the Current in a Single-Loop Circuit

Energy method to analyze electric circuits

The energy method

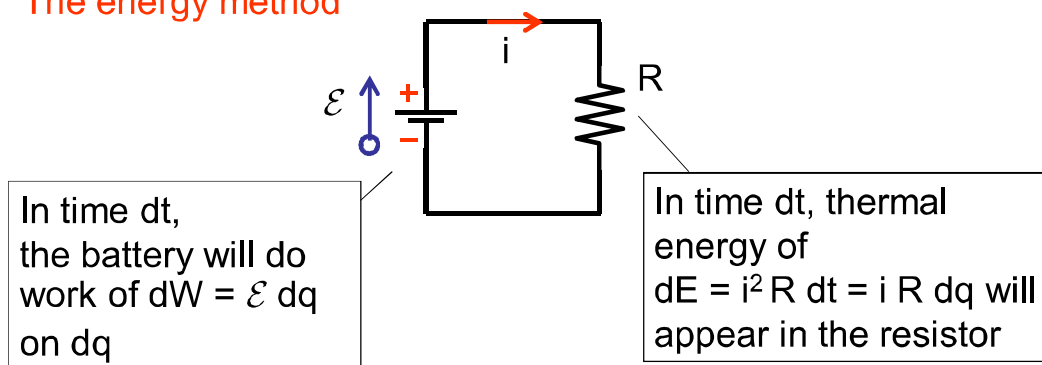

Energy is conserved

$$dW = dE$$

$$\mathcal{E} dq = i R dq$$

$$\mathcal{E} = i R$$

We will **not** use this method to analyze circuits


27-3 Calculating the Current in a Single-Loop Circuit

Potential method to analyze electric circuits

The potential method

Find the change in the electric potential as you move around the circuit.

Let us choose the clockwise direction.

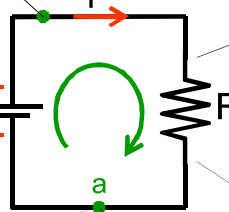

Thus the potential here is $V_a + \mathcal{E}$

As we move across the battery, the potential increases by \mathcal{E} because we are moving from lower to higher potential.

Let us start here at point a. Call the potential here V_a .

In a resistor, the current flows from higher to lower potential.

Higher potential


As we move across the resistor, the potential decreases by iR because we are moving from higher to lower potential.

Lower potential

The potential here is $V_a + \mathcal{E} - iR$.
But this is the same as V_a .
 $V_a + \mathcal{E} - iR = V_a$
 $+ \mathcal{E} - iR = 0$
 $\mathcal{E} = iR$

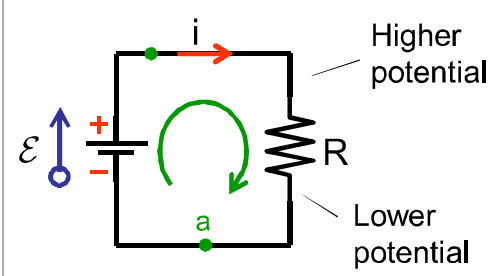27-3 Calculating the Current in a Single-Loop Circuit

Direction does not affect the final result



Higher potential


Lower potential

Change in potential for clockwise direction

$$V_a + \mathcal{E} - iR = V_a$$

$$+ \mathcal{E} - iR = 0$$

$$\mathcal{E} = iR$$

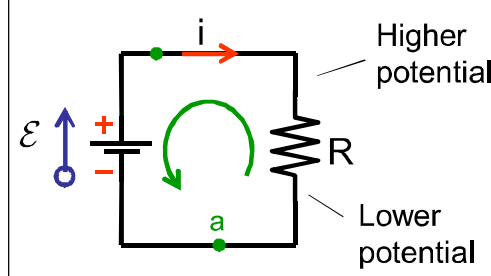

Higher potential

Lower potential

Change in potential for counterclockwise direction

$$V_a + iR - \mathcal{E} = V_a$$


$$+ iR - \mathcal{E} = 0$$

$$\mathcal{E} = iR$$

Direction does not affect the final result.

27-3 Calculating the Current in a Single-Loop Circuit

Loop rule

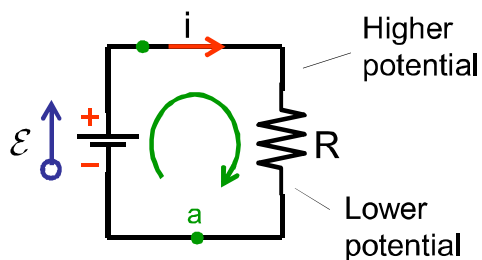

Loop rule (Kirchhoff's loop rule):


The algebraic sum of the changes in potential encountered in a complete traversal of any loop of a circuit must be zero.

$$\sum_{\text{loop}} \Delta V = 0$$




Conservation of energy

27-3 Calculating the Current in a Single-Loop Circuit

Signs convention

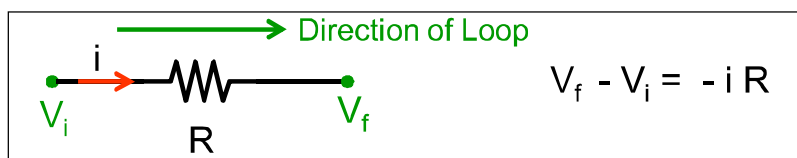


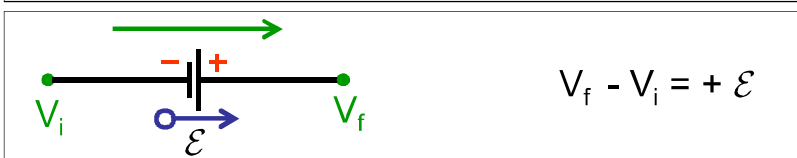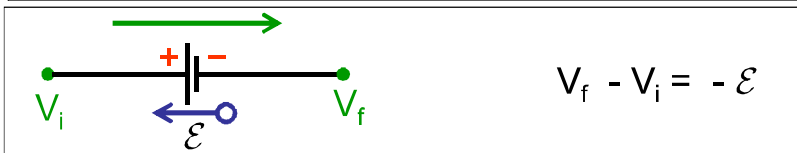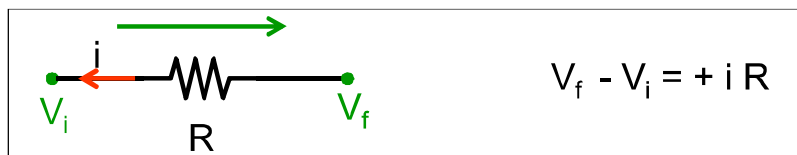In a resistor, the current flows from higher to lower potential.



27-3 Calculating the Current in a Single-Loop Circuit

Checkpoint 1

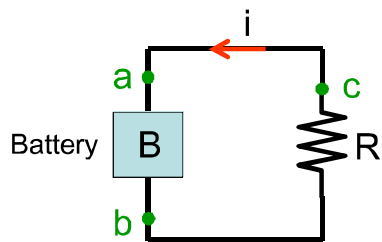

Draw the emf arrow

At points a, b, and c rank ...

the magnitude of current

the electric potential

the electric potential energy

Solution




All tie

$$V_b > V_a = V_c$$

$$U_b > U_a = U_c$$


27-3 Calculating the Current in a Single-Loop Circuit

Real battery

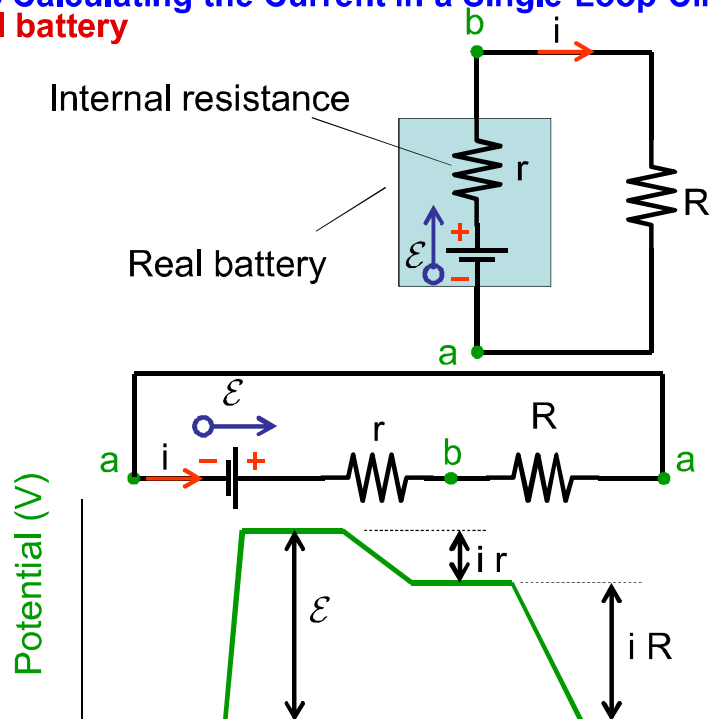

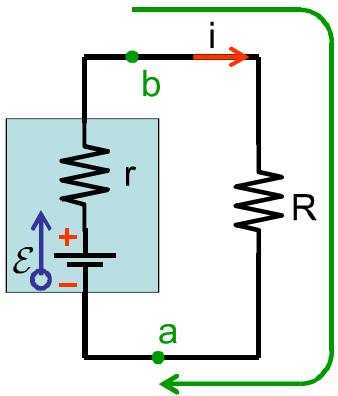27-4 Potential Differences


Potential difference does not depend on the path



$$V_b - iR = V_a$$

$$V_b - V_a = iR$$
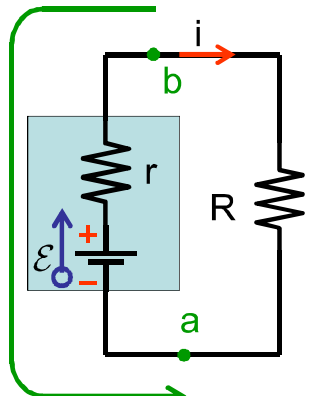
$$V_b - V_a = \frac{\varepsilon}{r+R} R$$



$$V_b + ir - \varepsilon = V_a$$

$$V_b - V_a = -ir + \varepsilon$$

$$= -\frac{\varepsilon}{r+R} r + \varepsilon$$

$$V_b - V_a = \frac{-\varepsilon r + \varepsilon r + \varepsilon R}{r+R}$$

$$V_b - V_a = \frac{\varepsilon}{r+R} R$$

The potential difference between any two points in a circuit does **not** depend on the path


27-4 Potential Differences

Potential difference across real battery

$$\varepsilon = 12 \text{ V}$$

$$r = 2 \Omega$$

$$R = 10 \Omega$$

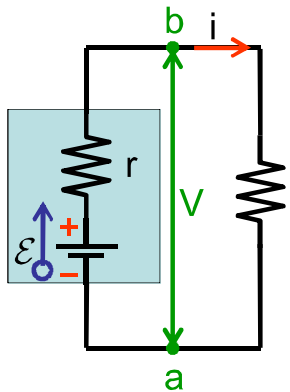


connected to a circuit

$$i = \frac{\varepsilon}{r+R} = \frac{12}{2+10} = 1 \text{ A}$$

$$V = \varepsilon - ir$$
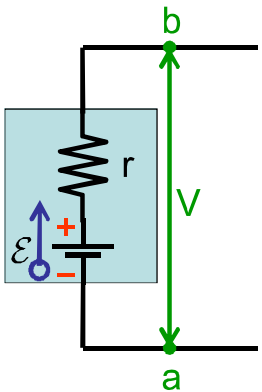
$$= 12 - 1(2) = 10 \text{ V} < \varepsilon$$



Not connected to a circuit




$$i = 0$$

$$V = \varepsilon - ir = \varepsilon = 12 \text{ V}$$

27-4 Potential Differences

Checkpoint 2

Compare \mathcal{E} and V

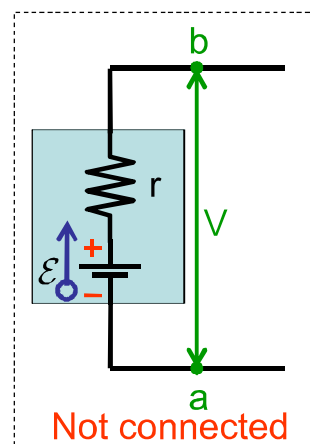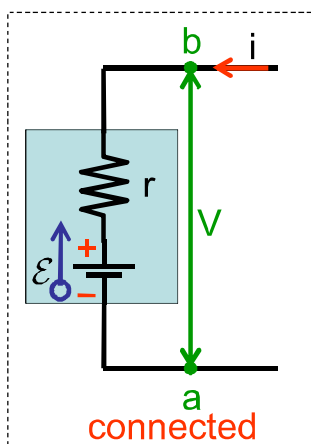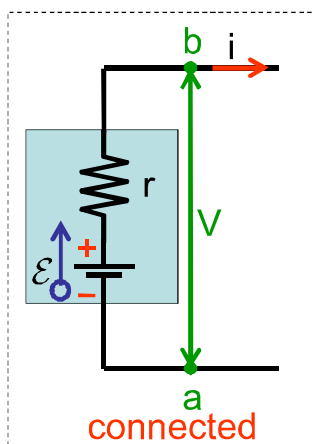

Solution

$$V = +\mathcal{E} - ir$$

$$V < \mathcal{E}$$

$$V = +\mathcal{E} + ir$$


$$V > \mathcal{E}$$

$$V = +\mathcal{E} + 0(r)$$

$$V = \mathcal{E}$$

27-4 Potential Differences

Power from real emf devices

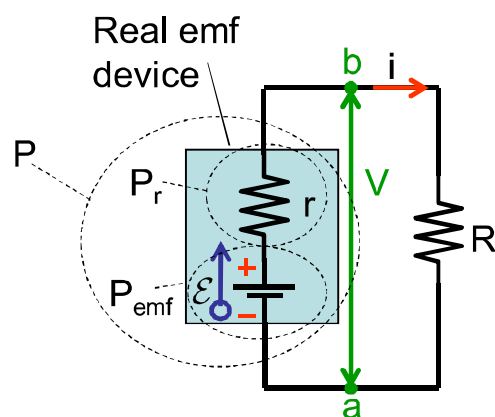

Rate of energy transfer from the real emf device to the charge carriers

$$P = iV$$

$$P = i(\mathcal{E} - ir)$$

$$P = i\mathcal{E} - i^2 r$$

$$P = P_{emf} - P_r$$

Electrons

Rate of energy transfer from the emf device to the charge carriers and to internal thermal energy

Rate of energy transfer to internal thermal energy


27-4 Potential Differences

Example 1

$$\mathcal{E}_1 = 4.4 \text{ V}, \mathcal{E}_2 = 2.1 \text{ V},$$

$$r_1 = 2.3 \, \Omega, r_2 = 1.8 \, \Omega, R = 5.5 \, \Omega.$$

What is the current in the circuit?

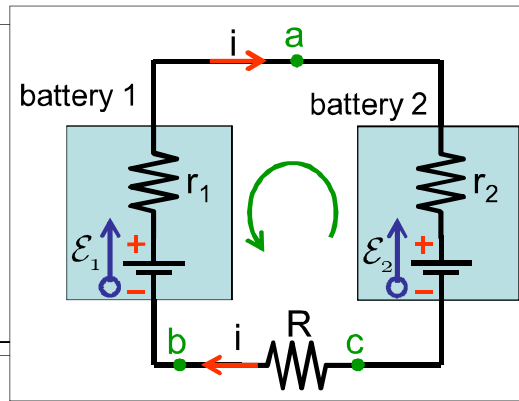

Solution

Pick any direction for the current.

Pick any direction for the loop rule.

$$i r_1 - \mathcal{E}_1 + i R + \mathcal{E}_2 + i r_2 = 0$$

$$i = \frac{\mathcal{E}_1 - \mathcal{E}_2}{r_1 + R + r_2} = 0.240 \text{ A} = 240 \text{ mA}$$

If your guess is wrong,
your current will be
negative.

27-4 Potential Differences


Example 2

$$\mathcal{E}_1 = 4.4 \text{ V}, \mathcal{E}_2 = 2.1 \text{ V},$$

$$r_1 = 2.3 \, \Omega, r_2 = 1.8 \, \Omega, R = 5.5 \, \Omega,$$

$$i = 240 \text{ mA}.$$

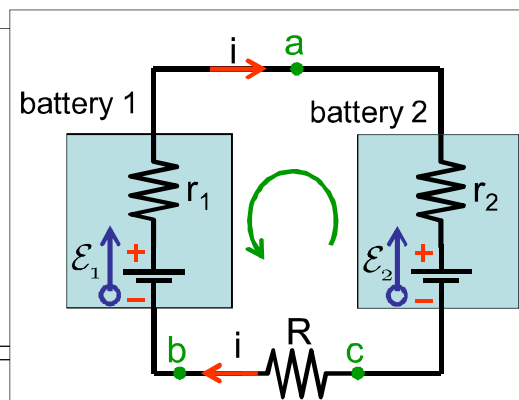What is the potential difference
between the terminals of battery 1?



Solution

$$V_a + i r_1 - \mathcal{E}_1 = V_b$$


$$V_a - V_b = -i r_1 + \mathcal{E}_1 = 3.84 \text{ V}$$

27-4 Potential Differences

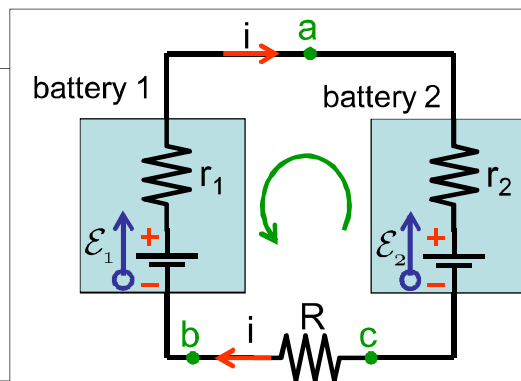Example 3


$$\begin{aligned}\mathcal{E}_1 &= 4.4 \text{ V}, \mathcal{E}_2 = 2.1 \text{ V}, \\ r_1 &= 2.3 \, \Omega, r_2 = 1.8 \, \Omega, R = 5.5 \, \Omega, \\ i &= 240 \text{ mA}.\end{aligned}$$

Redraw the circuit such that all the components are located on a horizontal line then plot the potential as a function of the location on the line.




Solution
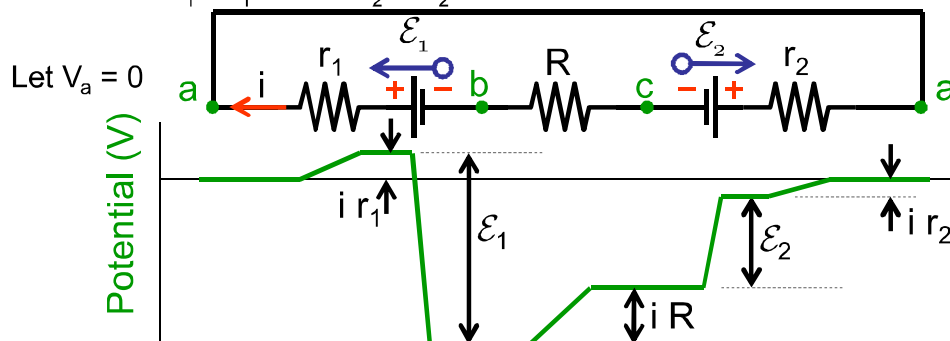
$$i r_1 - \mathcal{E}_1 + i R + \mathcal{E}_2 + i r_2 = 0$$



27-5 Resistances in Series and in Parallel

Resistances in series

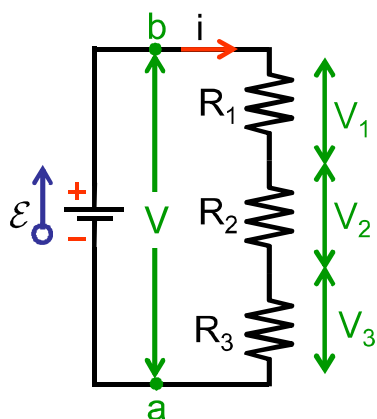

For steady flow of charge

Resistances in series

Resistances are wired one after another and a potential difference is applied to the two ends of the series.

The applied potential difference V is equal to the sum of the potential differences across all the resistances.


$$V = V_1 + V_2 + V_3$$

Since the charge is conserved, all the resistances have the same current i .

$$i = i_1 = i_2 = i_3$$

27-5 Resistances in Series and in Parallel

Formula - Resistances in series

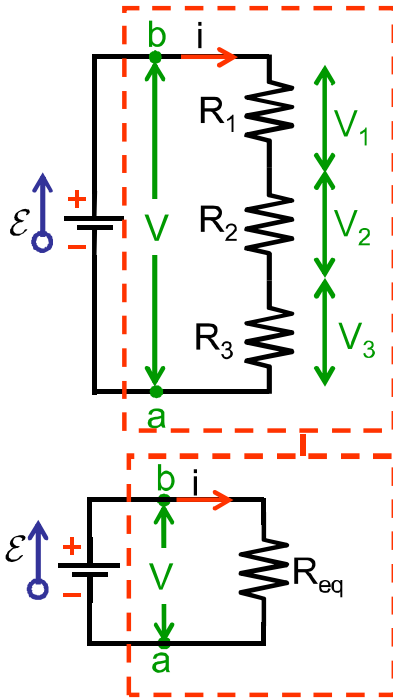

The equivalent resistance R_{eq} has **the same current**
 $i = i_1 = i_2 = i_3$
 and **the same total potential difference**
 $V = V_1 + V_2 + V_3$
 as the actual resistances.

Equivalent resistance


$$R_{eq} = R_1 + R_2 + R_3$$

$$R_{eq} = \sum_{j=1}^n R_j$$

For n resistances
in series

27-5 Resistances in Series and in Parallel

Derivation - Resistances in series

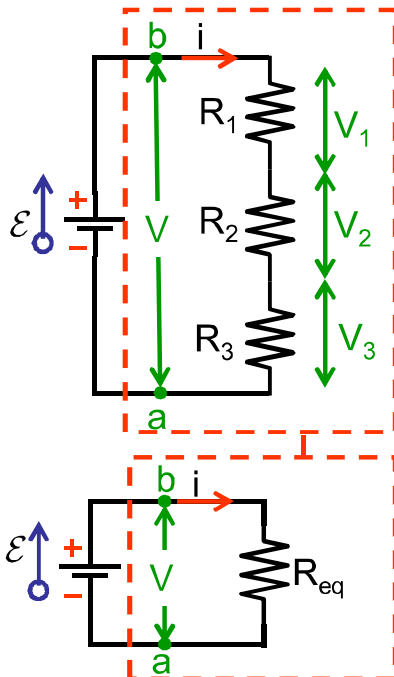

Derivation of $R_{eq} = R_1 + R_2 + R_3$


$$V = V_1 + V_2 + V_3$$

$$i R_{eq} = i R_1 + i R_2 + i R_3$$

$$R_{eq} = R_1 + R_2 + R_3$$

27-5 Resistances in Series and in Parallel

Resistances in parallel

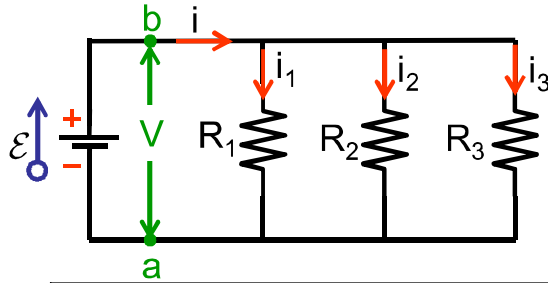

Resistances in parallel

Resistances are directly wired together on one side and directly wired together on the other side and a potential difference is applied across the pair of connected sides.

All the resistances have the same potential difference.

$$V = V_1 = V_2 = V_3$$


Since the charge is conserved, the total current passing through the resistances is equal to the sum of the current passing through each resistance.

$$i = i_1 + i_2 + i_3$$

For steady flow of charge

27-5 Resistances in Series and in Parallel

Formula - Resistances in parallel

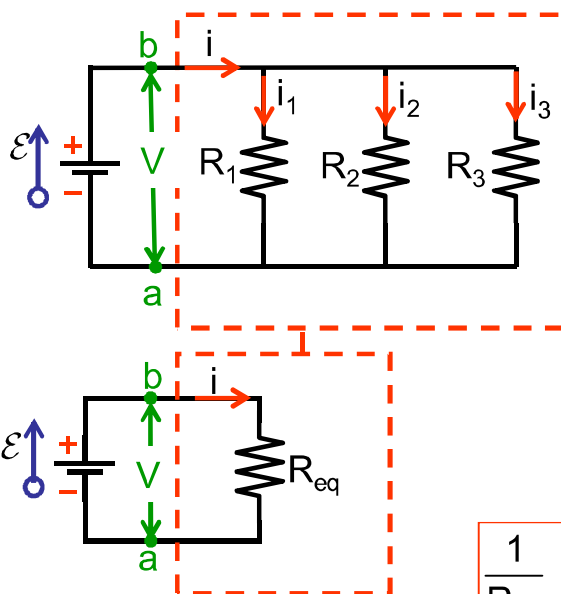

The equivalent resistance R_{eq} has the same total current

$$i = i_1 + i_2 + i_3$$

and the same potential difference

$$V = V_1 = V_2 = V_3$$

as the actual resistances

Equivalent resistance

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$\frac{1}{R_{eq}} = \sum_{j=1}^n \frac{1}{R_j}$$

For n resistances in parallel


R_{eq} is smaller than any of the actual resistances.

27-5 Resistances in Series and in Parallel

Derivation - Resistances in parallel

Derivation of
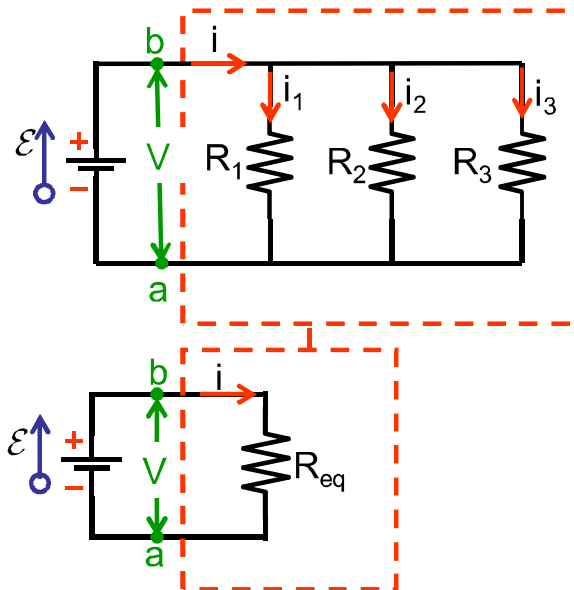
$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$





$$i = i_1 + i_2 + i_3$$

$$\frac{V}{R_{eq}} = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3}$$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

27-5 Resistances in Series and in Parallel

Comparison

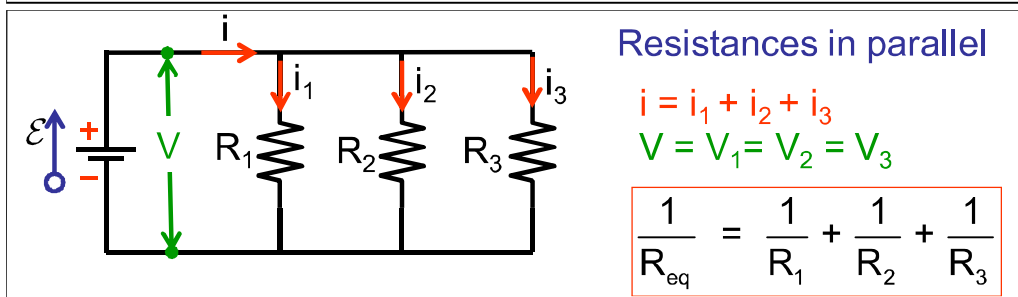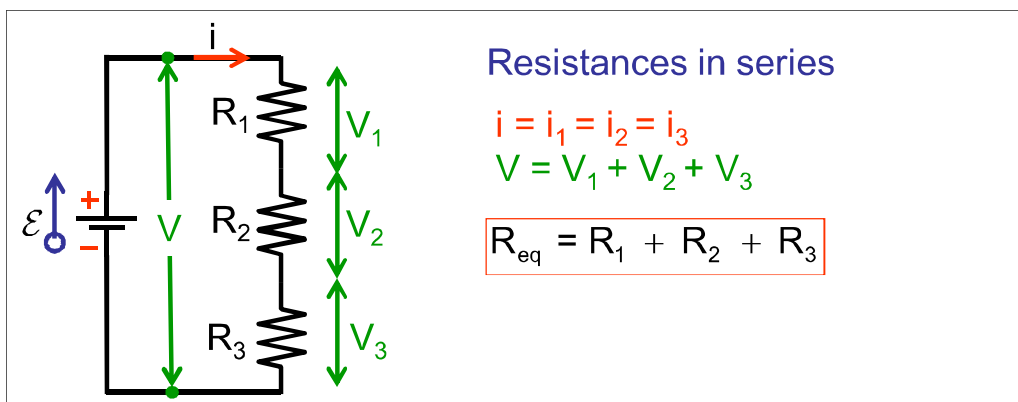


27-5 Resistances in Series and in Parallel

Example 4

$$\begin{aligned}\mathcal{E} &= 12 \text{ V}, \\ R_1 &= 20 \, \Omega, R_2 = 20 \, \Omega, \\ R_3 &= 30 \, \Omega, R_4 = 8.0 \, \Omega,\end{aligned}$$

What is the current through the battery?

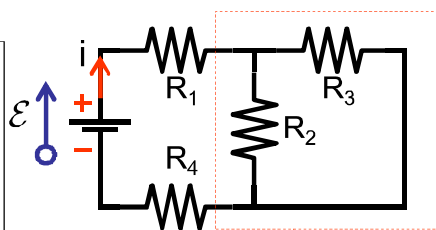


Solution

Simplify the circuit

$$R_{23} = \frac{R_2 R_3}{R_2 + R_3} = 12 \, \Omega$$

$$R_{2314} = R_1 + R_4 + R_{23} = 40 \, \Omega$$
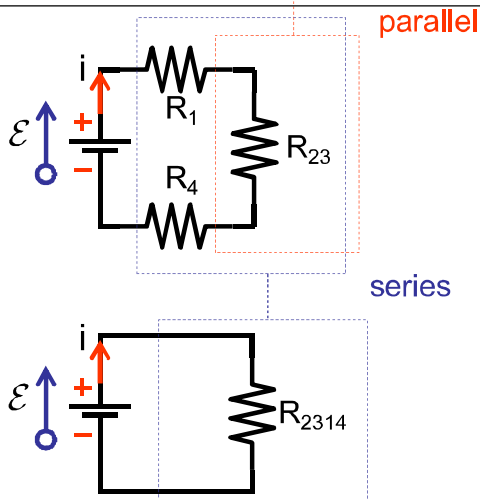
$$i = \frac{\mathcal{E}}{R_{2314}} = 0.3 \text{ A}$$




27-5 Resistances in Series and in Parallel

Example 5

$$\begin{aligned}\mathcal{E} &= 12 \text{ V}, \\ R_1 &= 20 \, \Omega, R_2 = 20 \, \Omega, \\ R_3 &= 30 \, \Omega, R_4 = 8.0 \, \Omega, \\ R_{23} &= 12 \, \Omega, i = 0.3 \text{ A}\end{aligned}$$

What is the current i_2 through R_2 ?

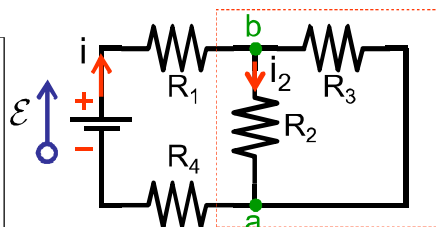

Solution


$$i_2 = \frac{V_{ba}}{R_2}$$

R_2 and R_3 are in parallel, potential differences across R_2 and R_{23} are equal.

R_1 , R_{23} and R_4 are in series, currents thorough R_{2314} and R_{23} are equal.

$$V_{ba} = R_{23} i = 3.6 \text{ V}$$

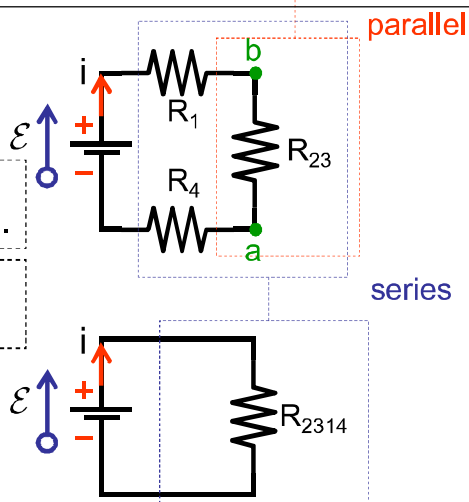
$$i_2 = \frac{V_{ba}}{R_2} = 0.18 \text{ A}$$



27-5 Resistances in Series and in Parallel

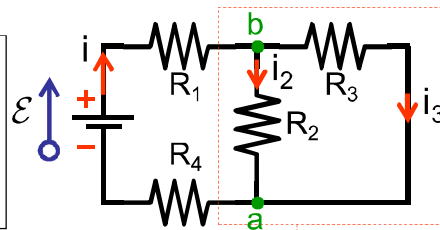Example 6

$\mathcal{E} = 12 \text{ V}$,
 $R_1 = 20 \Omega$, $R_2 = 20 \Omega$,
 $R_3 = 30 \Omega$, $R_4 = 8.0 \Omega$,
 $R_{23} = 12 \Omega$, $i = 0.3 \text{ A}$, $i_2 = 0.18 \text{ A}$, $V_{ba} = 3.6 \text{ V}$
 What is the current i_3 through R_3 ?




Solution

$$i_3 = \frac{V_{ba}}{R_3} = 0.12 \text{ A}$$

Another way


$$i = i_2 + i_3$$

$$i_3 = i - i_2 = 0.12 \text{ A}$$

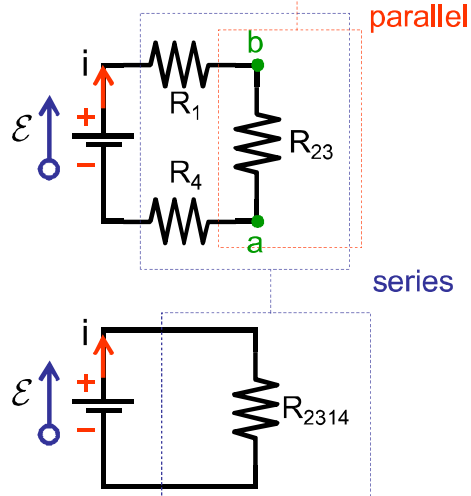

27-5 Resistances in Series and in Parallel

Checkpoint 3

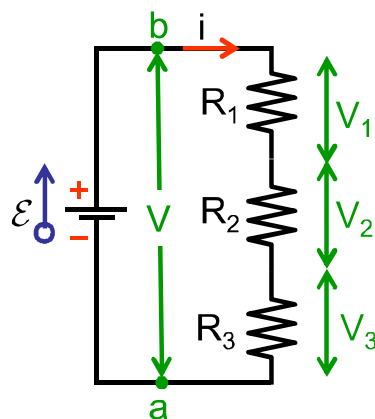

Let $R_1 > R_2 > R_3$

Rank ...

the current through the resistances

the potential difference across them


Solution

All tie

$$\begin{aligned}
 R_1 &> R_2 > R_3 \\
 i R_1 &> i R_2 > i R_3 \\
 V_1 &> V_2 > V_3
 \end{aligned}$$

27-6 Multiloop Circuits

Definitions

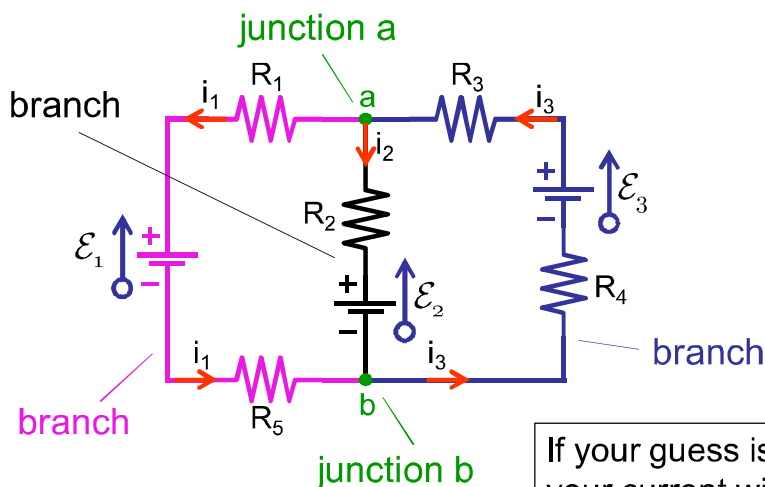


Pick any direction for the currents

If your guess is wrong, your current will be negative. The actual current is moving opposite to your guess.

Any point in a branch has the same current.

27-6 Multiloop Circuits

Junction rule

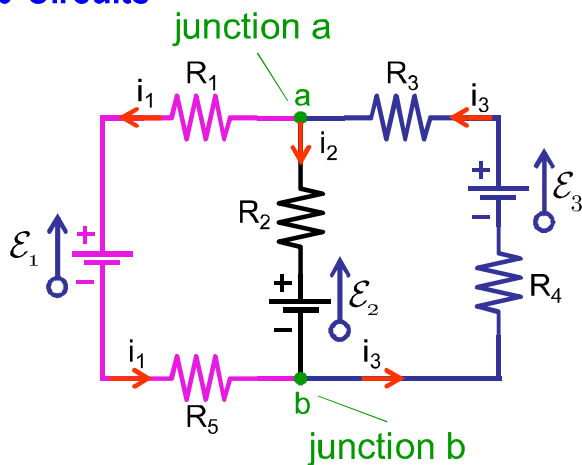

Junction rule (Kirchhoff's junction rule):


The sum of the currents entering any junction must be equal to the sum of the currents leaving that junction.

$$\sum_{\text{in}} i = \sum_{\text{out}} i$$

Conservation of charge
for steady flow of charge

27-6 Multiloop Circuits

Unknowns and independent equations

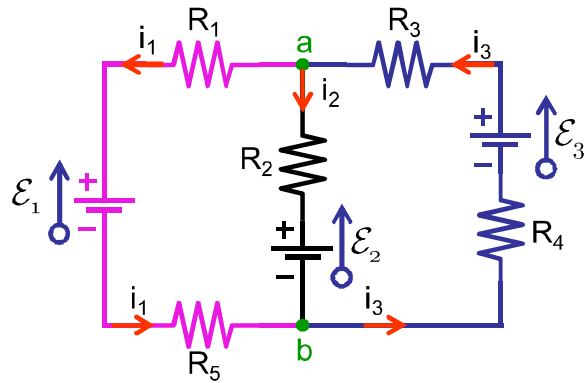

To analyze a circuit, we need to find as many **independent** equations as the number of unknowns in the circuit.


Suppose R 's and \mathcal{E} 's are given. we need to find i_1 , i_2 , and i_3

Number of unknowns = 3

Number of **independent** equations = 3

27-6 Multiloop Circuits

Illustration - Unknowns and independent equations

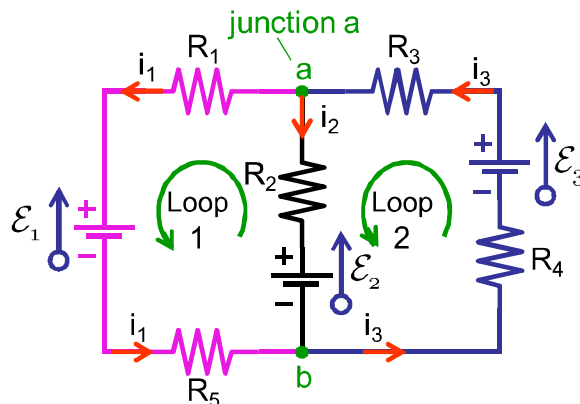

Junction rule at junction a

$$i_3 = i_1 + i_2$$

Loop rule on loop 1

$$-i_1 R_1 - \mathcal{E}_1 - i_1 R_5 + \mathcal{E}_2 + i_2 R_2 = 0$$

Loop rule on loop 2

$$-i_2 R_2 - \mathcal{E}_2 - i_3 R_4 + \mathcal{E}_3 - i_3 R_3 = 0$$


We have three unknowns and three independent equations

27-6 Multiloop Circuits

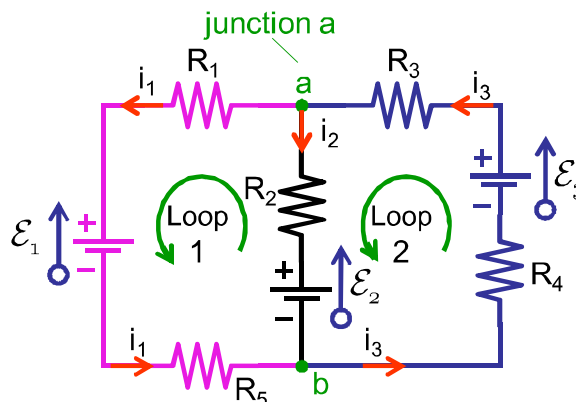Example 7

$$\begin{aligned}\mathcal{E}_1 &= 3.0 \text{ V}, \\ \mathcal{E}_2 &= \mathcal{E}_3 = 6.0 \text{ V}, \\ R_1 &= R_3 = R_4 = R_5 = 2.0 \, \Omega, \\ R_2 &= 4.0 \, \Omega.\end{aligned}$$

Find the magnitude and the direction of the current in each branch.



Solution

Junction rule at junction a

$$i_3 = i_1 + i_2$$

Loop rule on loop 1

$$\begin{aligned}-i_1 R_1 - \mathcal{E}_1 - i_1 R_5 + \mathcal{E}_2 + i_2 R_2 &= 0 \\ -4 i_1 + 3 + 4 i_2 &= 0\end{aligned}$$

Loop rule on loop 2

$$\begin{aligned}-i_2 R_2 - \mathcal{E}_2 - i_3 R_4 + \mathcal{E}_3 - i_3 R_3 &= 0 \\ -4 i_2 - 4 i_3 &= 0\end{aligned}$$

27-6 Multiloop Circuits

Example 7

Solution

$$i_3 = i_1 + i_2$$

$$-4 i_1 + 3 + 4 i_2 = 0$$

$$-4 i_2 - 4 i_3 = 0$$

Eliminate one variable, say i_3

$$-4 i_1 + 3 + 4 i_2 = 0$$

$$-4 i_2 - 4 (i_1 + i_2) = 0$$

$$-4 i_1 + 3 + 4 i_2 = 0$$

$$-8 i_2 - 4 i_1 = 0$$

$$-4 i_1 + 3 + 4 i_2 = 0$$

$$i_2 = -\frac{i_1}{2}$$

Eliminate another variable, say i_2

$$-4 i_1 + 3 + 4 \left(-\frac{i_1}{2}\right) = 0$$

$$-6 i_1 + 3 = 0$$

$$i_1 = 0.5 \text{ A}$$


$$i_2 = -0.25 \text{ A}$$

$$i_3 = 0.25 \text{ A}$$

27-6 Multiloop Circuits

Example 7

Solution

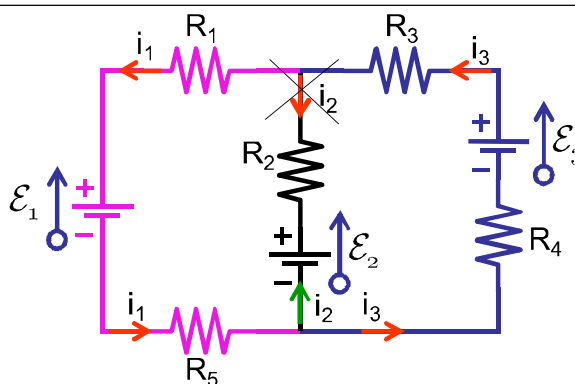

$$i_1 = 0.5 \text{ A}$$

$$i_2 = -0.25 \text{ A}$$


$$i_3 = 0.25 \text{ A}$$

Our guess for the direction of i_2 is wrong, it should be in the opposite direction.

Only after you finish finding all currents in a circuit, you can correct your guesses about directions.

27-6 Multiloop Circuits

Illustration - Dependent equation from a junction

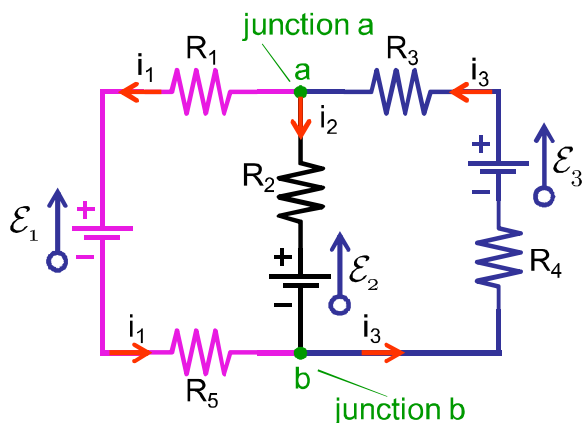

Junction rule at junction a

$$i_3 = i_1 + i_2$$

Junction rule at junction b

$$i_1 + i_2 = i_3$$


Same.

No new information.

These are not independent equations

27-6 Multiloop Circuits

Illustration - Dependent equation from loop

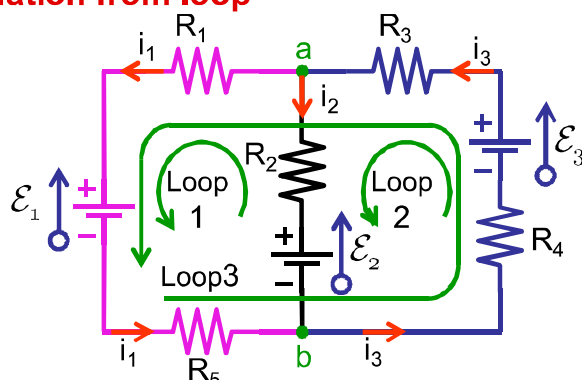

Loop rule on loop 1

$$-i_1 R_1 - \varepsilon_1 - i_1 R_5 + \varepsilon_2 + i_2 R_2 = 0$$

Loop rule on loop 2

$$-i_2 R_2 - \varepsilon_2 - i_3 R_4 + \varepsilon_3 - i_3 R_3 = 0$$

Add the two
equations

$$-i_1 R_1 - \varepsilon_1 - i_1 R_5 - i_3 R_4 + \varepsilon_3 - i_3 R_3 = 0$$

Loop rule on loop 3



Same as loop1 + loop 2.

No new information.

You can only use two of the three loops.

27-7 RC Circuits

Charging a capacitor

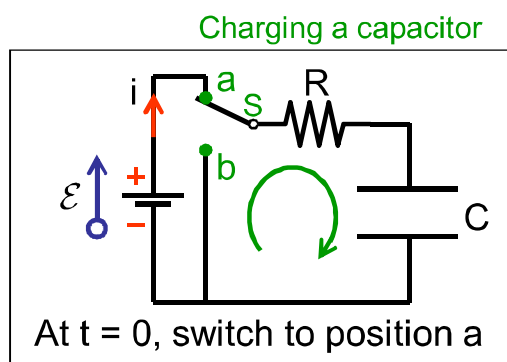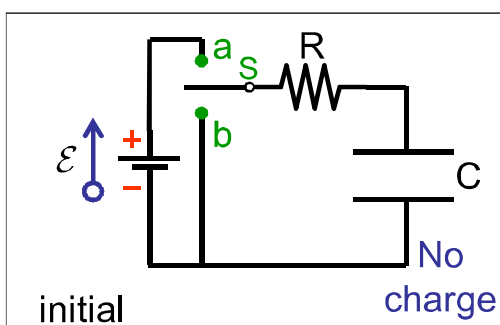

What is the charge on the capacitor as a function of time?

Loop rule

$$\varepsilon - i R - \frac{q}{C} = 0$$

$$\varepsilon - \frac{dq}{dt} R - \frac{q}{C} = 0 \quad \text{Differential equation}$$

At $t = 0$,	$q = 0$ and $i = \frac{\varepsilon}{R}$
--------------	---

At $t = \infty$,	$q = C\varepsilon$ and $i = 0$
-------------------	--------------------------------

27-7 RC Circuits

Formula - Charge on a capacitor while charging

Differential equation

$$\mathcal{E} - \frac{dq}{dt} R - \frac{q}{C} = 0$$


At $t = 0$, $q = 0$

At $t = \infty$, $q = C\mathcal{E}$

Solution



$$q = C\mathcal{E}(1 - e^{-t/RC})$$

While charging the capacitor

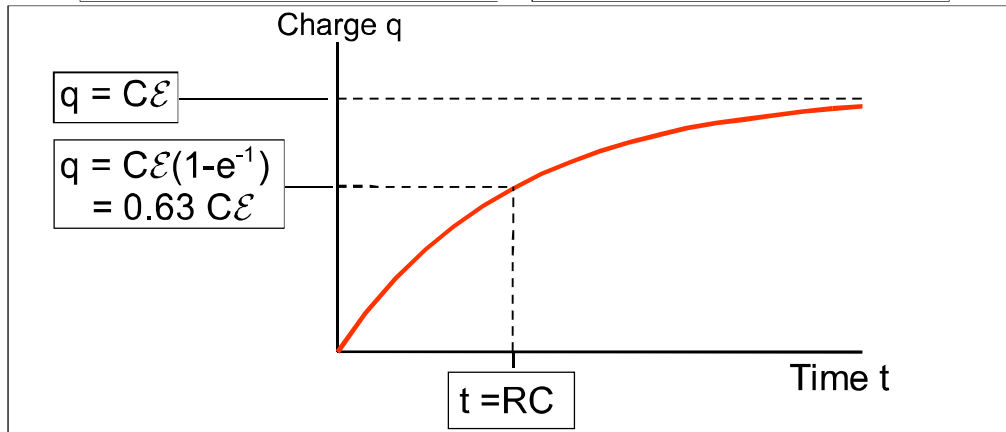

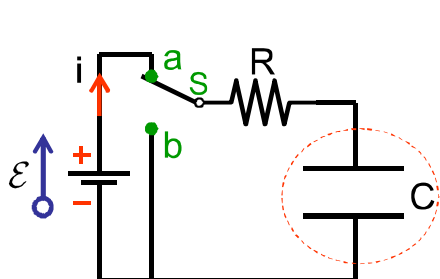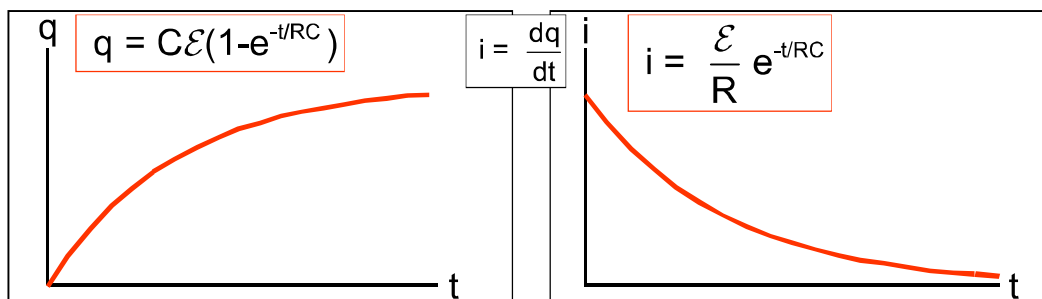27-7 RC Circuits

Formula - Current through a capacitor while charging



$t = 0, i = \frac{\mathcal{E}}{R}$


Initially, the capacitor acts as a connecting wire.

$t = \infty, i = 0$

finally, the capacitor acts as a broken wire.

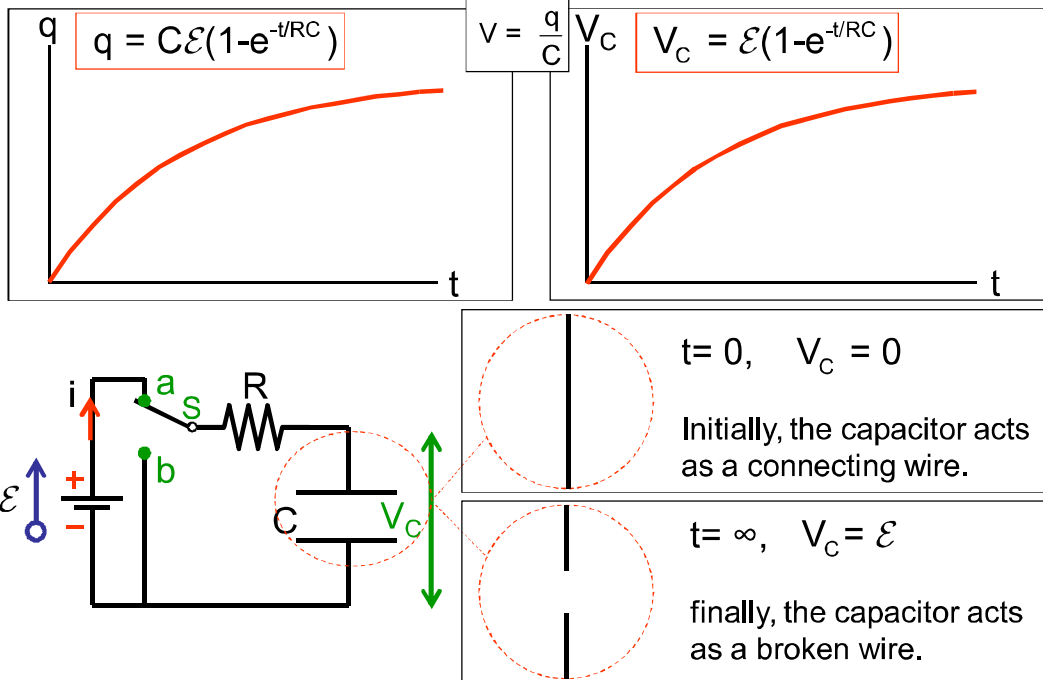27-7 RC Circuits

Formula - Potential difference across a capacitor while charging



27-7 RC Circuits

Time constant

RC has dimension of time

$$RC = \tau$$

RC = capacitive time constant

RC

Dimension similar to

$$\frac{V}{i} \frac{Q}{V} = \frac{Q}{i} = \frac{Q}{\frac{Q}{t}} = t$$

$$q = C\varepsilon(1 - e^{-t/RC}) = C\varepsilon(1 - e^{-t/\tau})$$

After one time constant

$$q = C\varepsilon(1 - e^{-1}) = 0.63 C\varepsilon$$

$$i = \frac{\varepsilon}{R} e^{-1} = 0.37 \frac{\varepsilon}{R}$$

$$V_C = \varepsilon(1 - e^{-1}) = 0.63 \varepsilon$$

τ pronounced tau

27-7 RC Circuits

Derivation - Charge on a capacitor while charging

Show that $q = C\mathcal{E}(1 - e^{-t/RC})$ is a solution of $\mathcal{E} - \frac{dq}{dt}R - \frac{q}{C} = 0$

At $t = 0$, $q = 0$

At $t = \infty$, $q = C\mathcal{E}$

Check the solution

$$\text{At } t = 0, \quad q = C\mathcal{E}(1 - e^{0/RC}) = C\mathcal{E}(1 - 1) = 0$$



$$\text{At } t = \infty, \quad q = C\mathcal{E}(1 - e^{-\infty/RC}) = C\mathcal{E}(1 - 0) = C\mathcal{E}$$

$$\frac{dq}{dt} = C\mathcal{E}\left(\frac{1}{RC} e^{-t/RC}\right) = \frac{\mathcal{E}}{R} e^{-t/RC}$$

$$\begin{aligned} \mathcal{E} - \frac{dq}{dt}R - \frac{q}{C} &= \mathcal{E} - \frac{\mathcal{E}}{R} e^{-t/RC} R - \frac{C\mathcal{E}(1 - e^{-t/RC})}{C} \\ &= \mathcal{E} - \mathcal{E} e^{-t/RC} - \mathcal{E}(1 - e^{-t/RC}) = 0 \end{aligned}$$

27-7 RC Circuits

Discharging a capacitor

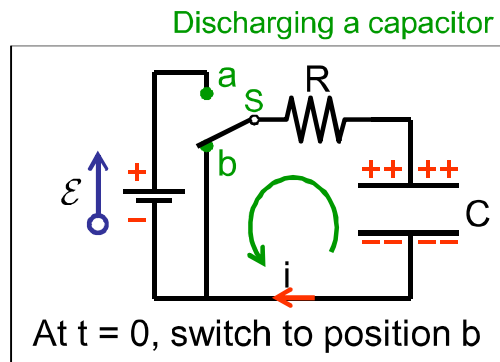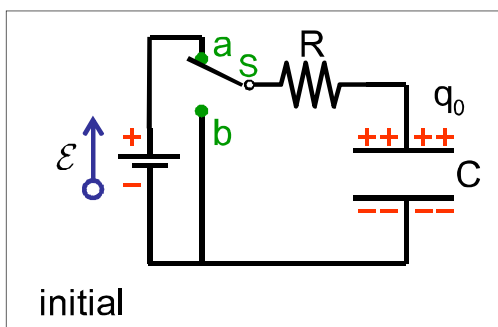


What is the charge on the capacitor as a function of time?

$$\frac{q}{C} + iR = 0$$

$$\frac{q}{C} + \frac{dq}{dt}R = 0 \quad \text{Differential equation}$$

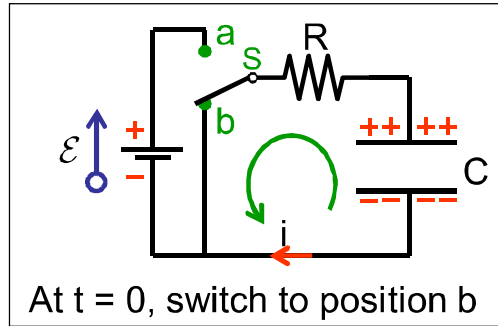27-7 RC Circuits

Formula - Charge on a capacitor while discharging



Differential equation

$$\frac{dq}{dt} R + \frac{q}{C} = 0$$

$$\text{At } t = 0, \quad q = q_0$$

$$\text{At } t = \infty, \quad q = 0$$


Solution

$$q = q_0 e^{-t/RC}$$

While discharging the capacitor

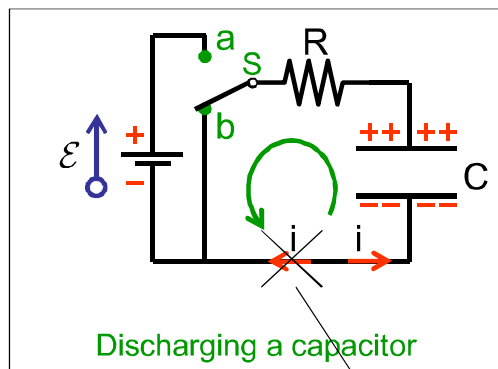27-7 RC Circuits

Formula - Current through a capacitor while discharging



$$q = q_0 e^{-t/RC}$$

$$i = \frac{dq}{dt}$$

$$i = -\frac{q_0}{RC} e^{-t/RC}$$


Our guess for the direction of the current is wrong

27-7 RC Circuits

Discharging after one time constant

$$q = q_0 e^{-t/RC}$$

$$i = \frac{q_0}{RC} e^{-t/RC}$$

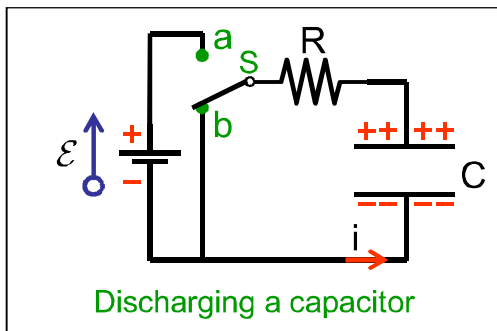

After one time constant

$$q = q_0 e^{-1} = 0.37 q_0$$

$$i = -\frac{q_0}{RC} e^{-1} = 0.37 \frac{q_0}{RC}$$

$$V_C = \frac{q_0}{C} e^{-1} = 0.37 \frac{q_0}{C}$$

27-7 RC Circuits

Example 8

In terms of RC , when will the charge on the capacitor be half its initial value?

Solution

$$q = q_0 e^{-t/RC}$$

$$\frac{1}{2} q_0 = q_0 e^{-t/RC}$$


$$\frac{1}{2} = e^{-t/RC}$$

$$\ln\left(\frac{1}{2}\right) = \ln(e^{-t/RC})$$

$$\ln(2) = \frac{t}{RC}$$

$$t = \ln(2)RC = 0.69 RC = 0.69 \tau$$

Discharging a capacitor

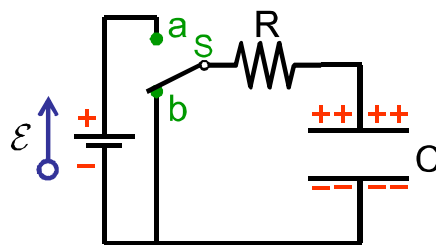

At $t = 0$, switch to position b

27-7 RC Circuits

Example 9

In terms of RC , when will the energy stored in the capacitor be half its initial value?

Solution

$$U = \frac{q^2}{2C} = \frac{q_0^2}{2C} e^{-2t/RC} = U_0 e^{-2t/RC}$$


$$\frac{1}{2} U_0 = U_0 e^{-2t/RC}$$

$$\frac{1}{2} = e^{-2t/RC}$$

$$\ln(2) = \frac{2t}{RC}$$

$$t = \frac{\ln(2)}{2} RC = 0.35 RC = 0.35 \tau$$

Discharging a capacitor

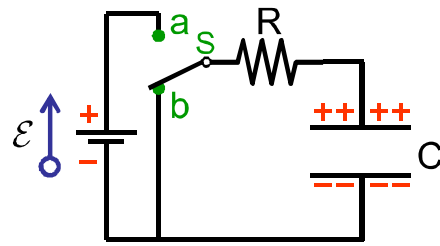

At $t = 0$, switch to position b

27-7 RC Circuits

Checkpoint 4


Rank the sets according to ...

A - initial current

B - time required for the current to decrease to its half its initial value

$\mathcal{E}(\text{V})$	$R(\Omega)$	$C(\mu\text{F})$
12	2	3
12	3	2
10	10	0.5
10	5	2

Charging a capacitor

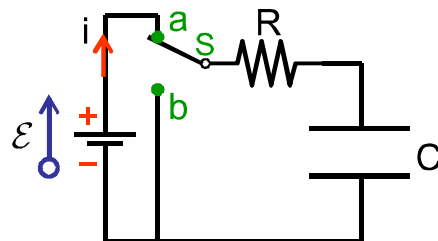

At $t = 0$, switch to position a

Solution

A	B
1	2
2	2
4	4
3	1

$$i = \frac{\mathcal{E}}{R}$$

$$t = 0.69 RC$$

$$i(t) = \frac{\mathcal{E}}{R} (1 - e^{-t/\tau}) \quad \tau = \frac{L}{R}$$

30-9 RL Circuits


Consider the circuit in the upper figure with the switch S in the middle position. At $t = 0$ the switch is thrown in position a and the equivalent circuit is shown in the lower figure. It contains a battery with emf \mathcal{E} , connected in series to a resistor R and an inductor L (thus the name " RL circuit"). Our objective is to calculate the current i as a function of time t . We write Kirchhoff's loop rule starting at point x and moving around the loop in the clockwise direction:

$$-iR - L \frac{di}{dt} + \mathcal{E} = 0 \rightarrow L \frac{di}{dt} + iR = \mathcal{E}$$

The initial condition for this problem is $i(0) = 0$. The solution of the differential equation that satisfies the initial condition is

$i(t) = \frac{\mathcal{E}}{R} (1 - e^{-t/\tau})$. The constant $\tau = \frac{L}{R}$ is known as the "**time constant**" of the RL circuit.

(30-18)

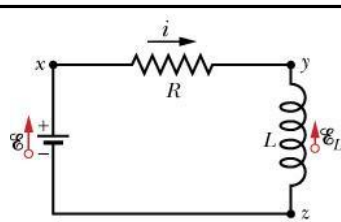

$$i(t) = \frac{\mathcal{E}}{R} (1 - e^{-t/\tau}) \quad \text{Here } \tau = \frac{L}{R}.$$

The voltage across the resistor $V_R = iR = \mathcal{E} (1 - e^{-t/\tau})$.

The voltage across the inductor $V_L = L \frac{di}{dt} = \mathcal{E} e^{-t/\tau}$.

The solution gives $i = 0$ at $t = 0$ as required by the initial condition. The solution gives $i(\infty) = \mathcal{E} / R$.

The circuit time constant $\tau = L / R$ tells us how fast the current approaches its terminal value:

$$i(t = \tau) = (0.632)(\mathcal{E} / R)$$

$$i(t = 3\tau) = (0.950)(\mathcal{E} / R)$$

$$i(t = 5\tau) = (0.993)(\mathcal{E} / R)$$

If we wait only **a few time constants** the current, for all practical purposes, has reached its terminal value (\mathcal{E} / R) .

(30-19)

