




Electromechanical Systems

001.0


Introduction

Dr Ezideen A Hasso


Phasors in AC Circuits

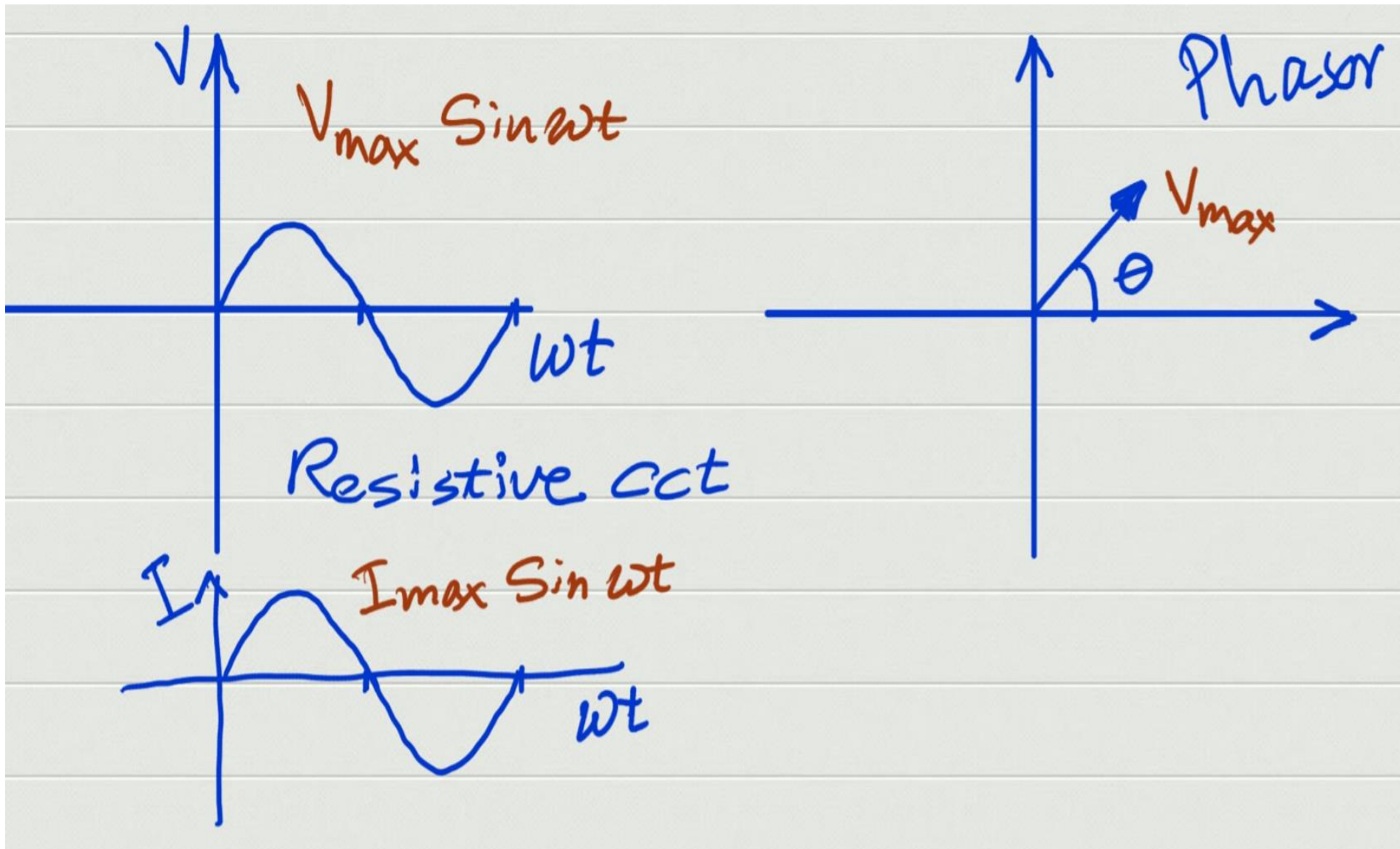

Inductive Load

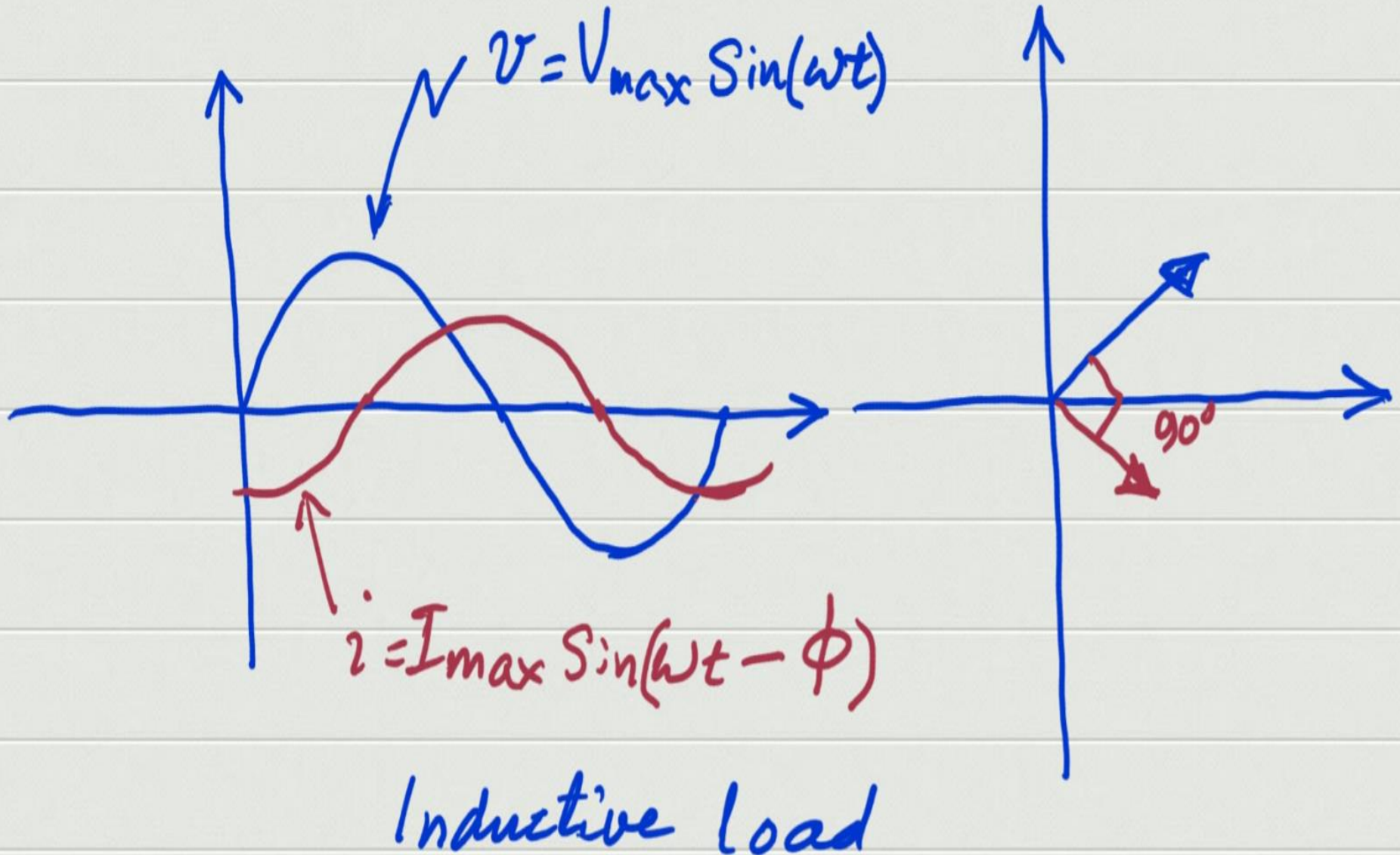

Capacitive Load

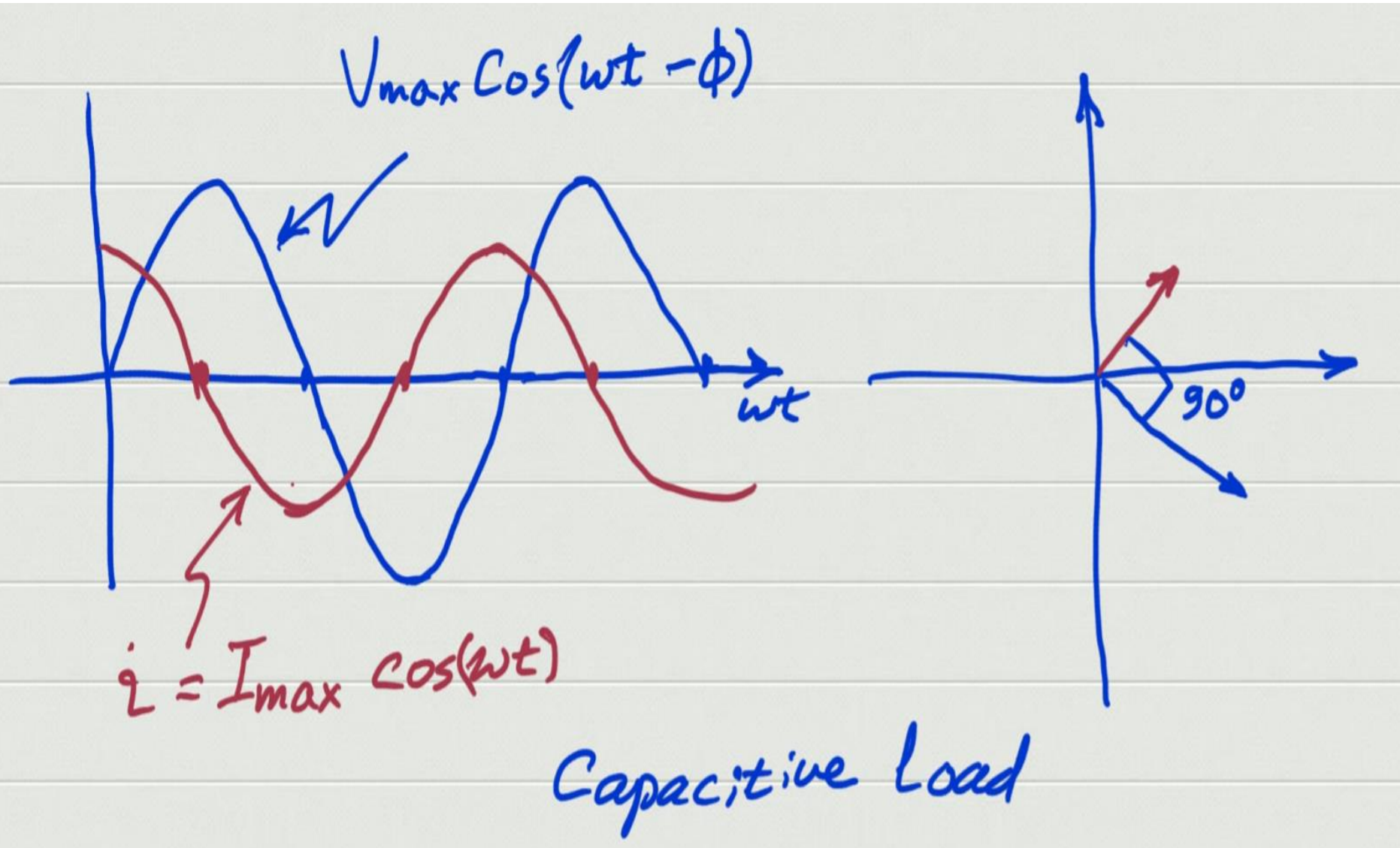

Reference Book

Principles of Electrical Machines and Power Electronics, P C Sen

Resistor $v = iR$

Inductor $v = L \frac{di}{dt}$, $i = \frac{1}{L} \int v dt$

Capacitor $i = C \frac{dv}{dt}$, $v = \frac{1}{C} \int i dt$

Euler Formula

$\left. \begin{matrix} e^x \\ e^{-x} \end{matrix} \right\} \rightarrow$ what is special about this?

When we take the derivative of this function we get a scaled function of the original

$$\bullet \frac{d}{dx}(e^x) = e^x \quad \leftarrow \text{same function}$$

$$\bullet \frac{d}{dt}(e^{\tau t}) = \tau e^{\tau t} \quad \leftarrow \text{scaled function}$$

$$e^{jx} = \cos(x) + j \sin(x)$$

$$e^{-jx} = \cos(x) - j \sin(x)$$

$$\cos(x) = \frac{e^{jx} + e^{-jx}}{2}$$

$$\sin(x) = \frac{e^{jx} - e^{-jx}}{2j}$$

Reference Book



Principles of Electrical Machines and Power Electronics, P C Sen

Reference Book


A.C. Circuits

Ohm's law
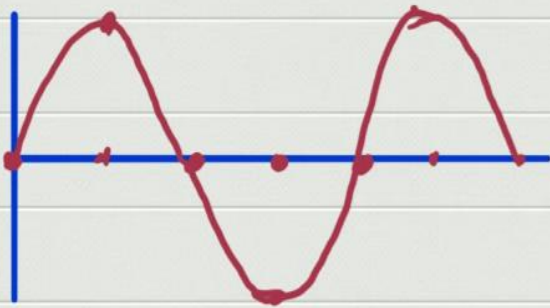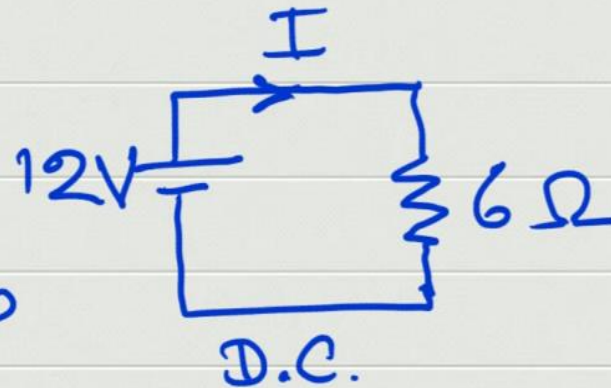
$$I = \frac{V}{R} = \frac{12}{6} = 2 \text{ Amp}$$



$$emf = - \frac{d\phi}{dt}$$

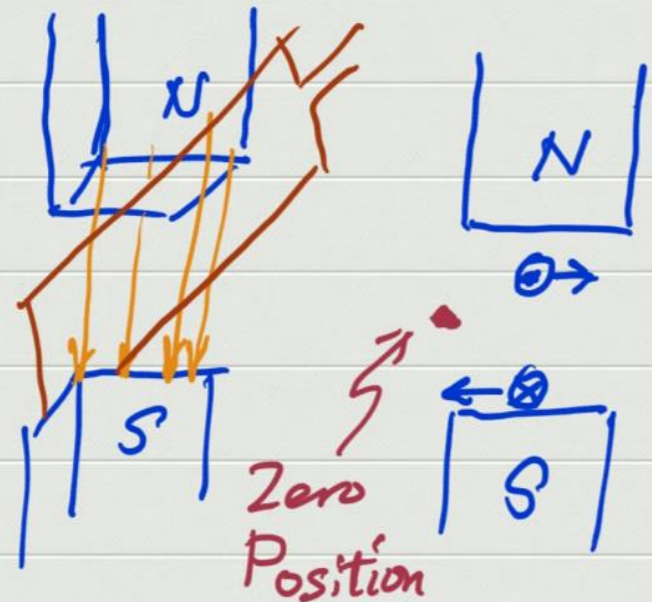

Half Wave Rectifier

