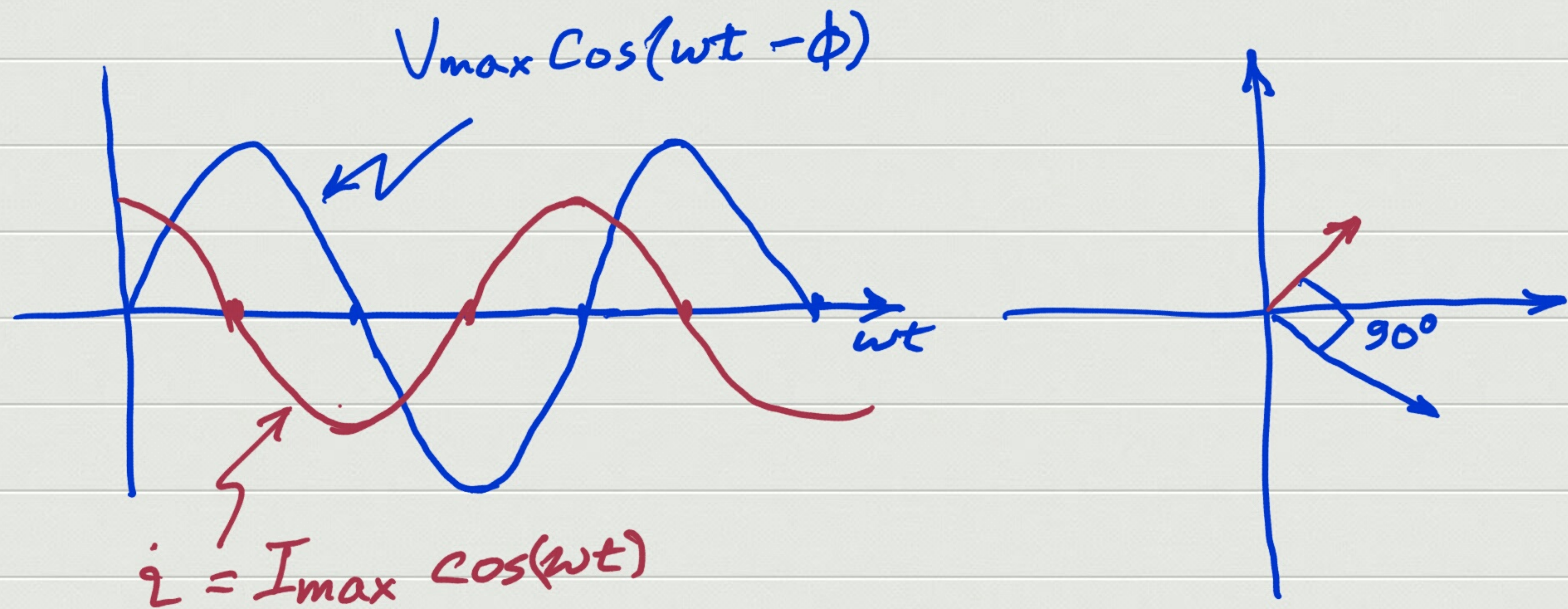


$$i = I_{\max} \sin(\omega t - \phi)$$

Inductive load



Capacitive Load

Ref: Principles of Electrical Machines
and Power Electronics
P.C. Sen

Resistor $v = iR$

Inductor $v = L \frac{di}{dt}$, $i = \frac{1}{L} \int v dt$

Capacitor $i = C \frac{dv}{dt}$, $v = \frac{1}{C} \int i dt$

Euler Formula

$\left. \begin{matrix} e^x \\ e^{-x} \end{matrix} \right\} \rightarrow$ What is special about this?

When we take the derivative of this function we get a scaled function of the original

$$\bullet \frac{d}{dx}(e^x) = e^x \quad \swarrow \text{same function}$$

$$\bullet \frac{d}{dt}(e^{\lambda t}) = \lambda e^{\lambda t} \quad \swarrow \text{scaled function}$$

$$e^{jx} = \cos(x) + j \sin(x)$$

$$e^{-jx} = \cos(x) - j \sin(x)$$



$$\cos(x) = \frac{e^{jx} + e^{-jx}}{2}$$

$$\sin(x) = \frac{e^{jx} - e^{-jx}}{2j}$$


A.C. Circuits

Ohm's law
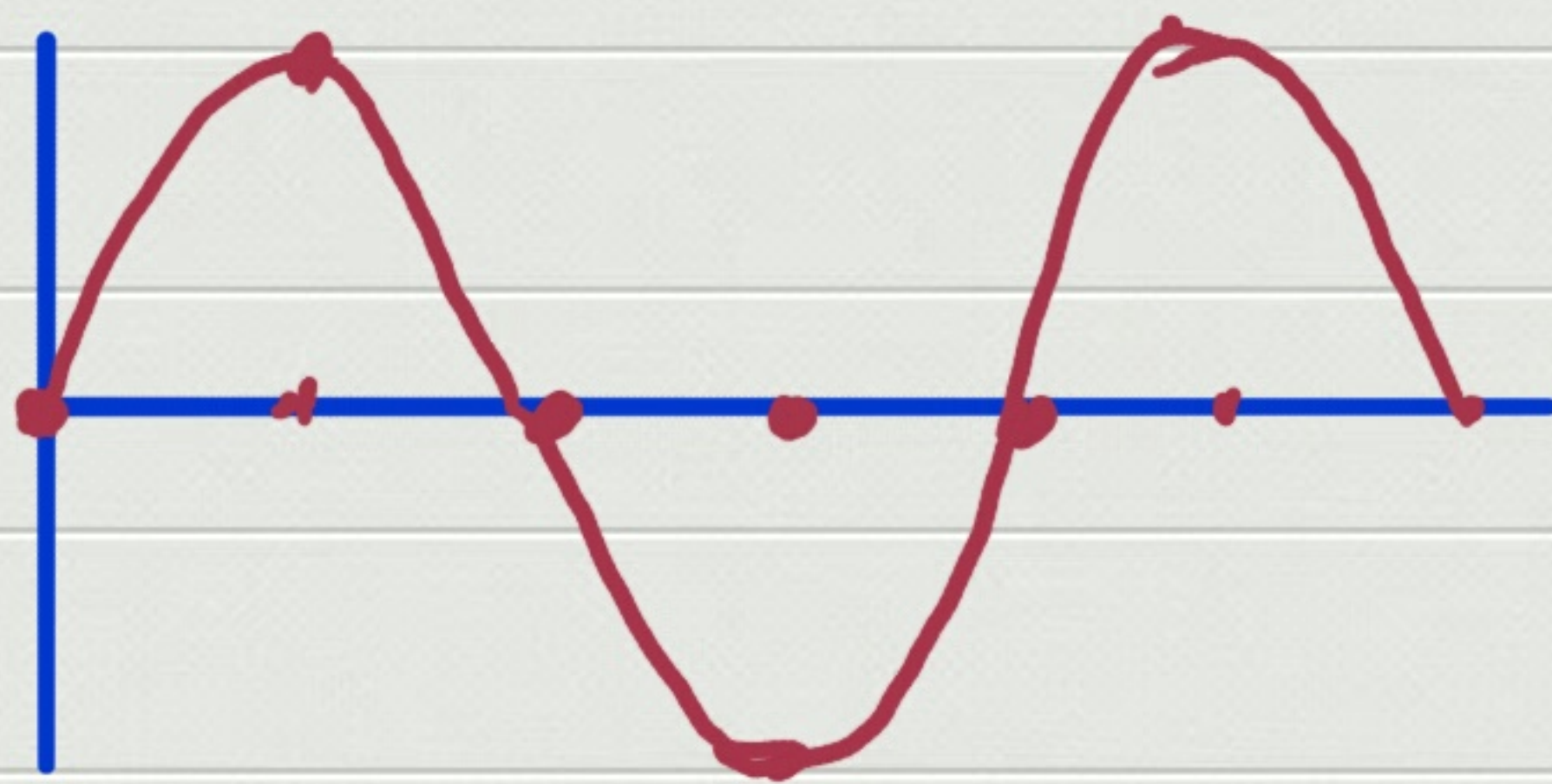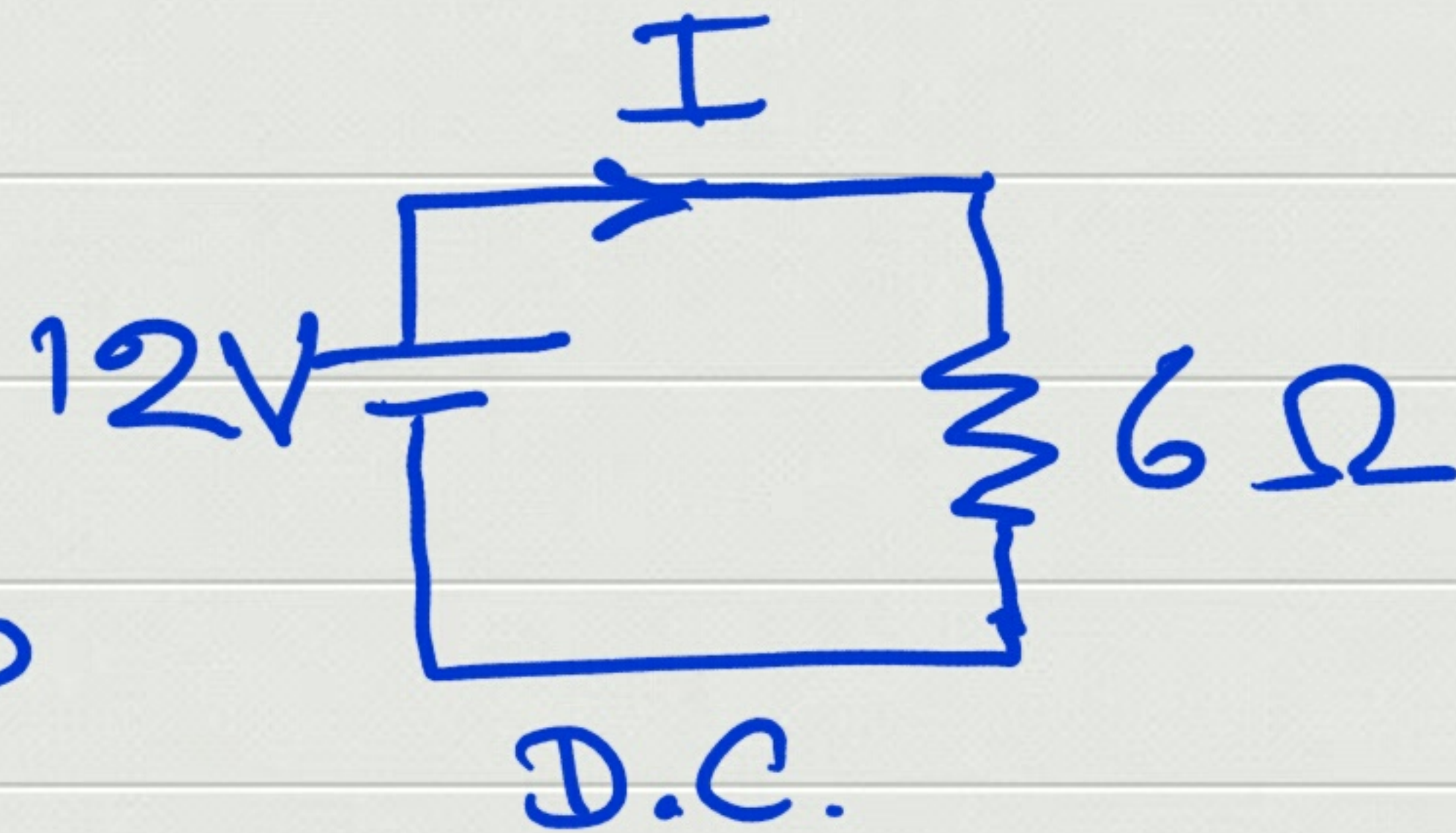
$$I = \frac{V}{R} = \frac{12}{6} = 2 \text{ Amp}$$



$$emf = - \frac{d\phi}{dt}$$

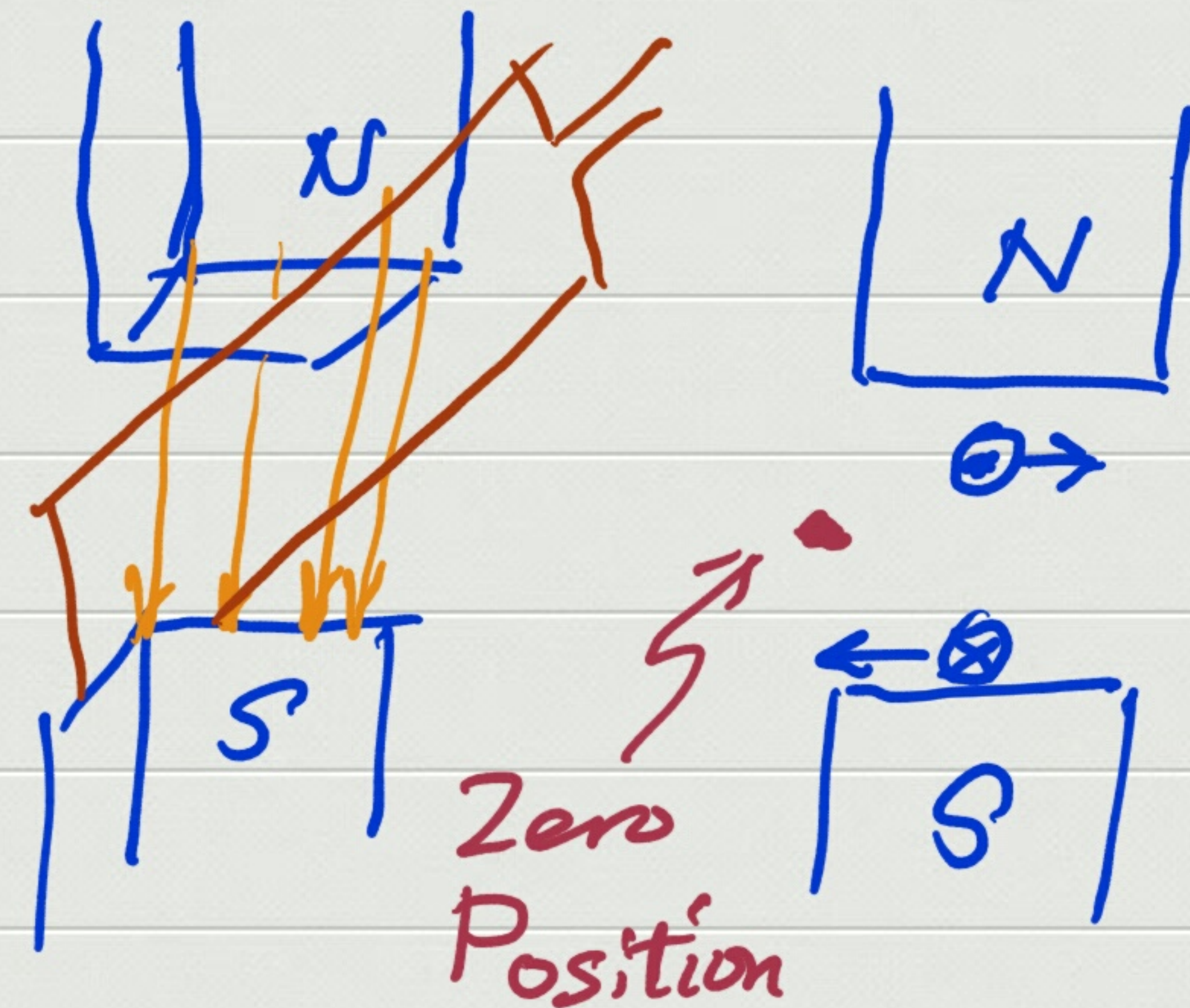

Power

$$v = V_{\max} \sin(\omega t)$$

$$i = I_{\max} \sin(\omega t)$$

$$P = v \times i$$



for a resistive circuit;

$$v = iR \quad \& \quad i = \frac{v}{R}$$

$$P = i^2 R \quad \underline{\text{or}} \quad \frac{v^2}{R}$$

$$P = \frac{(V_{\max} \sin(\omega t))^2}{R}$$
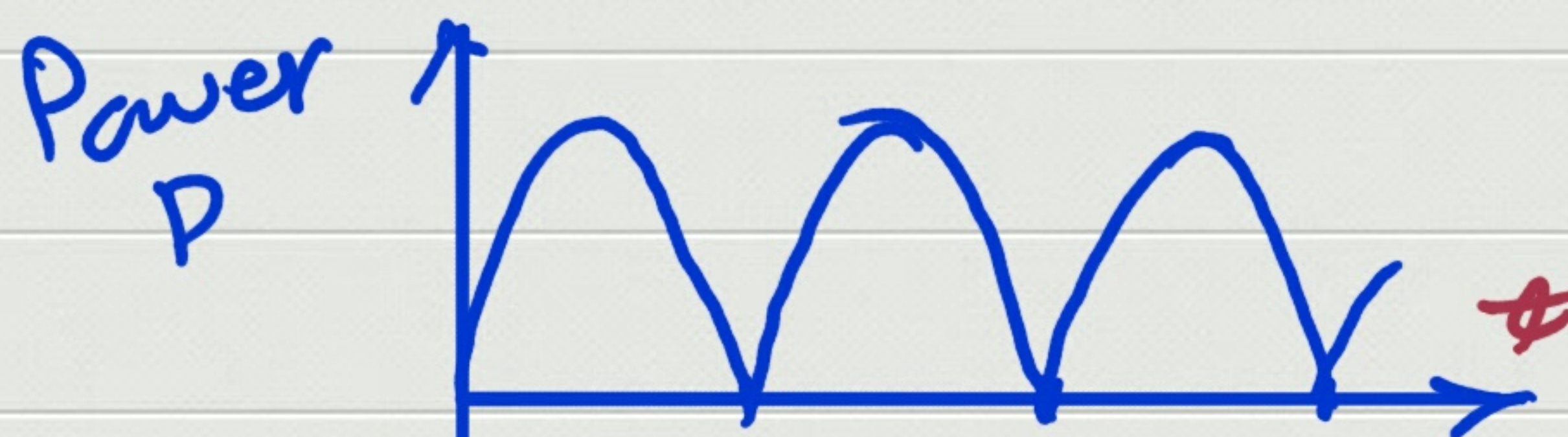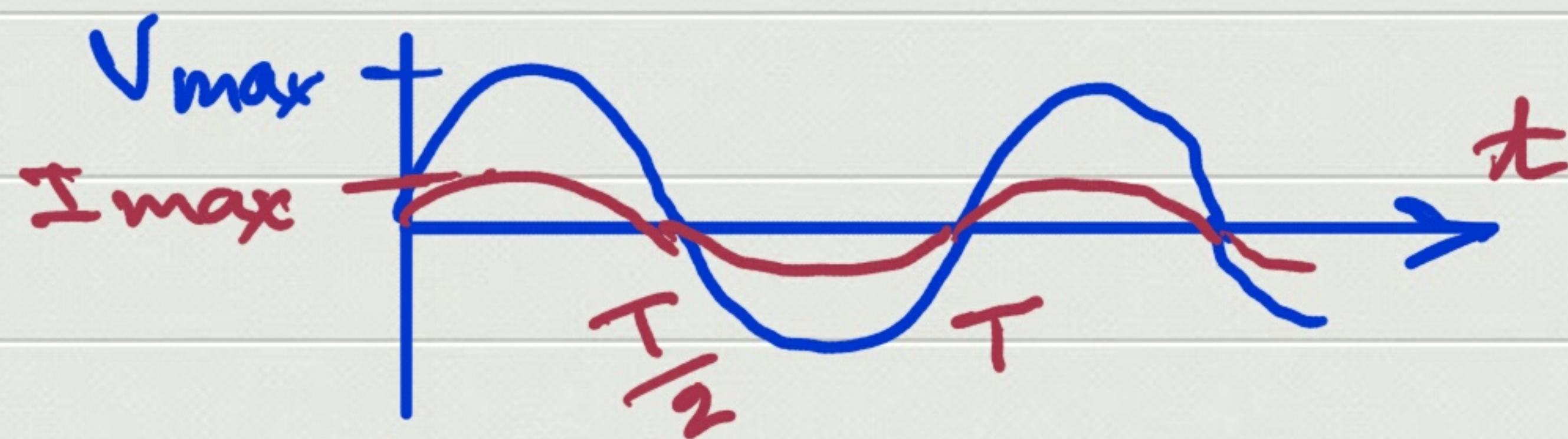
$$\underline{\text{or}} \quad P = (I_{\max} \sin(\omega t))^2 R$$



$$P = (I_{\max}^2 R) \sin^2(\omega t)$$

Scaler
value

$$\omega = 2\pi f \\ = \frac{2\pi}{T}$$

$$\textcircled{a} \text{ } \underline{t=0}, \omega t = \frac{2\pi}{T} \times 0, \sin^2(0) = \underline{0}$$

$$\textcircled{a} \text{ } \underline{t=\frac{T}{4}}, \omega t = \frac{2\pi}{T} \cdot \frac{T}{4} = \frac{\pi}{2}, \sin^2\left(\frac{\pi}{2}\right) = (1)^2 = \underline{1}$$

$$\textcircled{a} \text{ } \underline{t=\frac{T}{2}}, \omega t = \frac{2\pi}{T} \cdot \frac{T}{2} = \pi, \sin^2(\pi) = \underline{0}$$

$$\textcircled{a} \text{ } \underline{t=\frac{3T}{4}}, \omega t = \frac{2\pi}{T} \cdot \frac{3T}{4} = \frac{3}{2}\pi, \sin^2\left(\frac{3}{2}\pi\right) = \underline{1}$$

$$\textcircled{a} \text{ } \underline{t=T}, \omega t = \frac{2\pi}{T} \cdot T = 2\pi, \sin^2(2\pi) = \underline{0}$$

so this $P(t)$ instantaneous value! Average Power?


$$P_{\text{ave}} = \frac{1}{T} \int_0^T P(t) dt$$

$$= \frac{2}{T} \int_0^{T/2} P(t) dt$$

$$P(t) = P_{\text{max}} \sin^2(\omega t)$$

$$P_{\text{max}} = I_{\text{max}}^2 R$$

$$= \frac{2}{T} \cdot P_{\text{max}} \cdot \int_0^{T/2} \sin^2(\omega t) dt$$



$$\frac{P_{\text{max}}}{2}$$

The average of $\sin^2(\omega t)$ over a whole cycle is 0.5

$$P_{\text{ave}} = \frac{I_{\text{max}}^2 R}{2}$$

or

$$= \frac{V_{\text{max}}^2}{2R}$$

This is valid for any alternating current supply

Root Mean Square (RMS)

$$P_{ave} = \frac{V_{rms}^2}{R} = \frac{V_{max}^2}{2R}$$

$$V_{rms}^2 = \frac{V_{max}^2}{2}$$

$$V_{rms} = \frac{V_{max}}{\sqrt{2}}$$

$$V_{rms} = 0.707 V_{max}$$

$$I_{rms} = ?$$

$$P_{ave} = I_{rms}^2 \cdot R = \frac{I_{max}^2 R}{2}$$

$$\underline{\text{or}} \quad I_{rms} = \frac{I_{max}}{\sqrt{2}}$$


$$I_{rms} = 0.707 I_{max}$$

for the 220 Volt RMS
the $V_{max} = 310$ Volt

Why RMS ?

AC v DC

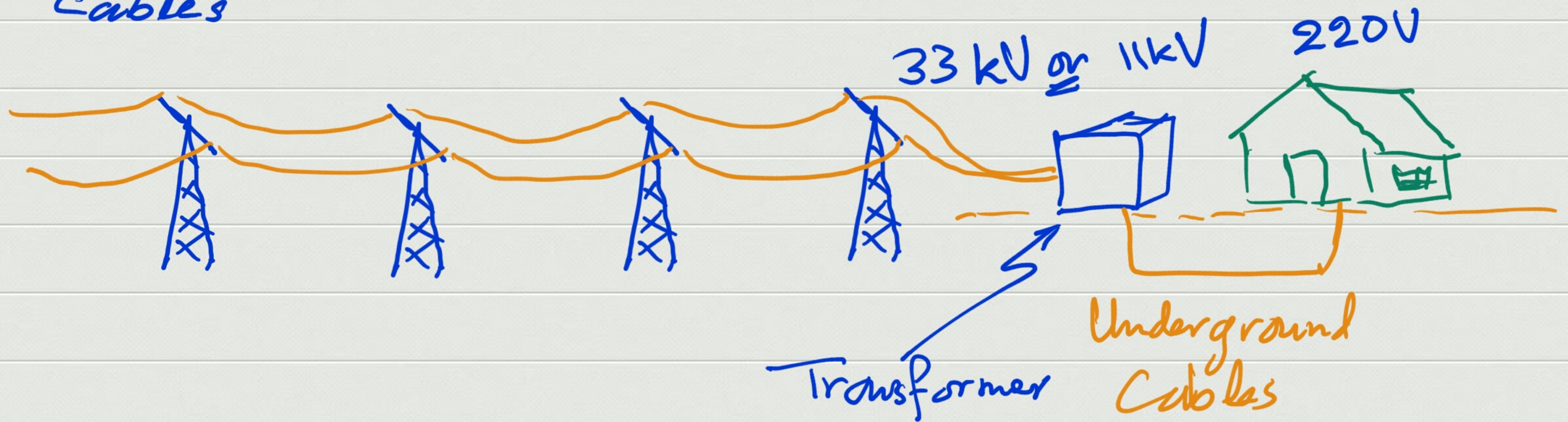
It was Tesla's idea to change from D.C. to A.C. to minimize transmission loss in cables



Coil

$$v_1 = \frac{d\phi}{dt}$$

per one turn,
for N_1 turns

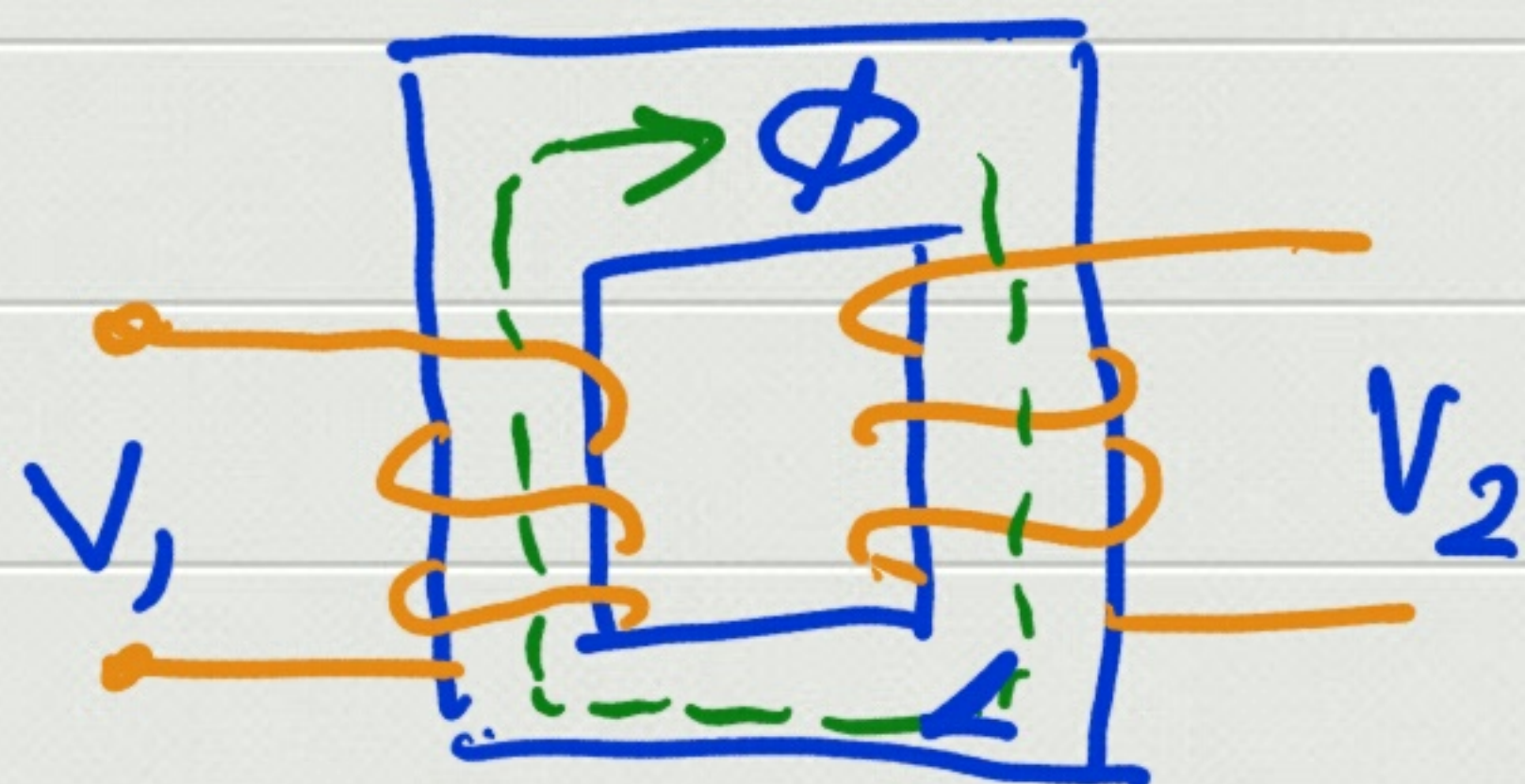

$$V_1 = N_1 \frac{d\phi}{dt}$$

Same

$$V_2 = N_2 \frac{d\phi}{dt}$$

$$\frac{V_1}{V_2} = \frac{N_1}{N_2}$$

Power in both
sides of the Trans.
are the same;

$$i_1 V_1 = i_2 V_2$$

$$\frac{V_1}{V_2} = \frac{i_2}{i_1} = \frac{N_1}{N_2}$$

1 MW ac & d.c. system
220V & for a.c. 33kV
(1- ϕ) cable resist. R

$$P = 1 \text{ MW} = V_{ac} i_{ac} = V_{dc} i_{dc}$$

$$33 \times 10^3 \times i_{ac} = 10^6$$

$$i_{ac} = \frac{1000}{33} = 30 \text{ A}$$

Power loss in cables:

$$P = i^2 R \times 2$$

$$= 30^2 \times 2 \times R$$

$$= 1800 R$$

$$= 1.8 \times 10^3 R$$

$$P = V_{dc} I_{dc}$$

$$10^6 = 220 \times I_{dc}$$

$$I_{dc} = \frac{1,000,000}{220}$$


$$= 4545 \text{ A}$$

$$P = I^2 \times 2 \times R$$


$$= 41 \times 10^6 R$$

Ratio is 23,000

Half wave rectifier

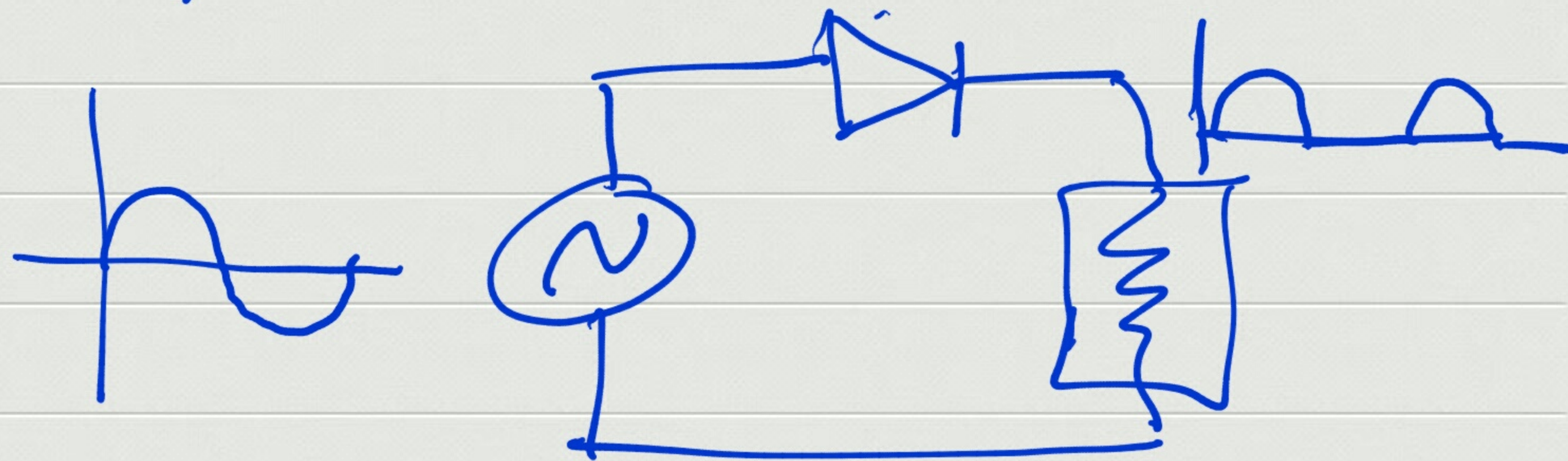

Full wave rectifier

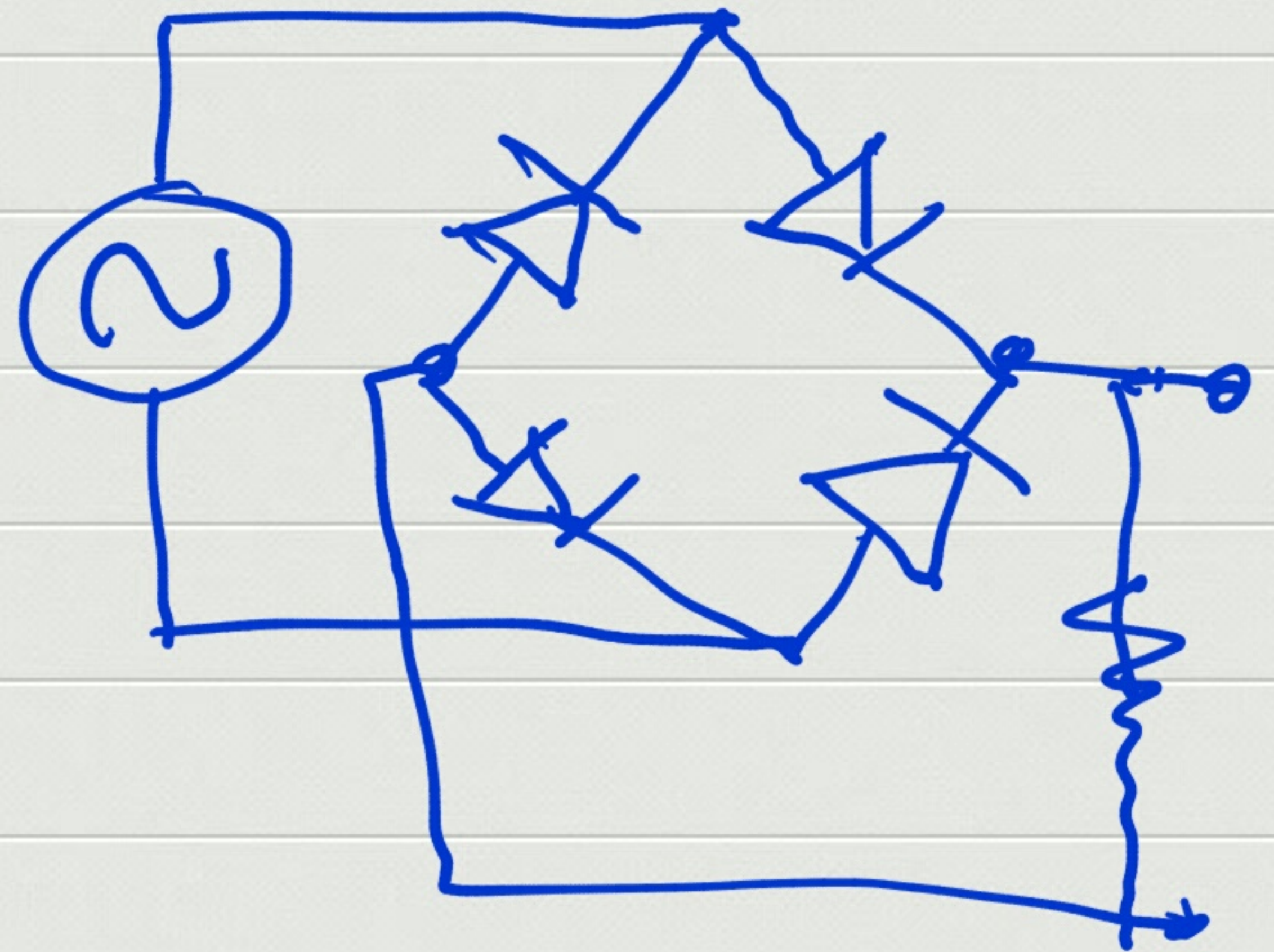

TISHK WORKSHOP

PIS

(Courses
Section

Dept
TI — Grade

Coordinator
for shared
courses

(Management/
ADD student